

QUALITIES OF A COLOUR RECEIVING/VIDEO CAMERA TECHNICIAN

02

1. A good CIV/video camera ^{technician} must be fully acquainted with the theory of colour metric, the tri-colour kinescope and accessory and the assembly of colour circuit.
2. He should note that diagnosing CIV trouble is an exercise in training, logic, patience, and the use of the senses, looks magazine articles. ~~the~~ Manufacturer service notes are available or a source of knowledge.
3. Self discipline is needed to take advantage of the information on the regular basis.
4. The experienced technician should learn often the hard way that he must look, listen, smell and feel before he leaps to conclusion.
5. He should note that CIV is more complex to service than its black & white counterpart.
6. The experienced service man have to check overall receiver performance first on the basis of the receiving as a black and white set, only when the technician is satisfied that the b/w TV performance is satisfactory, will he view a colour picture.
7. ~~He~~ He will then note whether colour are tuned and remain locked in sync.
8. The failure in colour are carefully analysed using all senses, looking for indicating an overrated resistor, a fine which crack in the...

VERTICAL SYNC PROBLEMS.

The lack of vertical sync or a very critical vertical sync can be caused by improper adjustment of controls, as well as by defective circuits.

The first step in troubleshooting this symptom is to adjust the vertical hold (sometimes called vertical back or vertical sync) control.

There is no problem if vertical sync can be obtained with the vertical hold control at mid range.

3 If the vertical hold control must be full or (near full) or it is necessary to readjust the control frequently, there is a problem in the vertical sync circuits.

4 If the problem cannot be cured by adjustment, check for the presence of proper sync pulses at the input to the vertical sweep circuit at the primary of the transformer.

5 Then check the Sawtooth Sweep portion of the vertical oscillator at the base of ^{first} transistor. The vertical pulses will appear to rise on the sawtooth.

6 If the sync pulses are normal and it is impossible to get proper vertical sync, the most likely causes are:

Leaking by pass capacitors C5, C6 in the vertical sweep unit.

Worn vertical hold control.

Leaking or defective vertical oscillator transistor.

Defective vertical transformer (leakage winding or some similar imaginary defect).

65
If the low-voltage power supply is completely inoperative (or almost zero) the screen can be dark. If the low-voltage supply is low, the picture will be decentered. Of course in either case, the sound is absent or abnormal. On the other hand, if the horizontal oscillator and drive circuits are defective, there will be no high voltage or horizontal sweep.

If either high voltage or the boost voltage is absent or abnormal, this will isolate the trouble to the corresponding cat. If both voltages are absent or absent (with the drive signal good) the problem is in horizontal output transistor or video line capacitor or video amplifier.

If the ^{high} voltage is absent, check for ac at the anode side of the high voltage rectifier. Observe all the usual precautions when measuring high voltage. In addition do not make any test of the high voltage with solid circuits. The transient voltages can damage the transistors.

DARK SCREEN BUT SOUND NORMAL.

It is likely that the following(s) is/are responsible for the above fault.

1. horizontal output
2. high voltage circuit
3. Picture tube can also be defective.
4. lack of filament voltage
5. Open, shorted or leaking capacitors
6. leaking horizontal output transistor
7. Open or shorted diodes
8. Defective flyback transformer.

~~NOT~~

Picture Overscan.

The picture becomes dim even with the brightness fully on, and there is abnormal enlargement of the picture or raster.

(1) In some circuits, the brightness control operates in reverse, rotating the control for an increase in brightness produces a decrease!

(2) If the picture overscan is not accompanied by sufficient well (a symptom of horizontal output failure) the cause is a failure in the high voltage circuit only.

(3) Any circuit problem that reduces (but does not completely eliminates) the high voltage output to the picture tube second anode can cause overscan.

The general likely defects are ~~being~~

1. leaking high voltage capacitor.

2. defective high voltage tube and rectifiers

3. leaking high voltage leads

4. defect in high voltage circuit protective resistance (if any)

5. Shorted turns in high voltage winding of the flyback transformer.

6. If the high voltage is low, check any high voltage filter capacitors for leakage.

7. Many colour television ~~picture~~ pictures and raster bloom when both brightness and contrast controls are turned fully up. This is an inherent design problem (lack of high voltage regulation).

Poor Purity, improper convergence adjustments, a shift in the ~~front~~ gray scale tracking and other colour section defects permits colour to appear on the receiver screen during monochrome reception.

To clear this critical adjustment, the technician must examine the entire screen to observe the effect of each control as the changes the setting.

The difficulty and inconvenience of the task if station programme material is used for observation, can be easily imagined, why the technician is attempting to

concentrate on specific areas the picture is changing in contrast, brightness and contrast.

Pattern generator with stable, fixed pattern in black and white is best to be used for convergence because colour fringing is more noticeable on black and white programme.

Finally colour fringing is most apparent when mostly of the screen is dark and only a small percentage is illuminated with dots or bars.