

ANALOGUE ELECTRONICS IV

EEEC 434

LECTURE NOTES ON

(Principles of operation, classification, ^{construction} and characteristics of oscillators)


2005

2

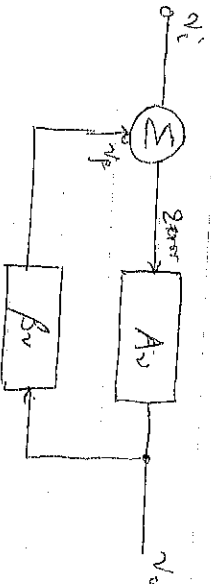(1)

Positive feedback concept

One of the characteristics of an oscillator is that it must have a positive feedback which leads to high gain, a possibility of oscillation. Below is a block diagram of an amplifier with positive feedback.



It has been shown that

$$A_{vf} = \frac{A_v}{1 - A_v B_v} \quad \text{eqn (1)}$$

Criteria for oscillations

1) The Barkhausen Criterion must be satisfied, that is:

$$A/B = 1$$

If $AB < 1$, oscillation will not occur & will cease to occur. If $AB > 1$, a near-pure sine wave is not achieved.

2) The frequency at which a sustained oscillation will operate is the frequency for which the total phase shift introduced as a signal passes from the input terminals, through the amplifier and feedback network, and back again to the input, is precisely zero (or in terms multiples of 2π). Or simply, the frequency of a sustained oscillation is determined by the condition that the loop phase shift is zero.

from eqn 1, when $AB = 1$

$$A_{vf} = \frac{A_v}{1-1} = \frac{A_v}{0} = \infty$$

$$\text{Since } A_{vf} = \frac{A_v}{0} = \frac{V_o}{V_i}$$

It can be analysed to mean that there will be an output even without input (i.e. $V_i = 0$). It becomes an

(2)

Oscillator (Signal generator)

Oscillators (Introduction)

Many electronic devices require a source of energy at a specific frequency from low Hz to several MHz. This is only achieved by a device called oscillator. The output waveform of oscillator may be sinusoidal, triangular (saw tooth), pulse, square wave depending on application. They can be used to generate high frequency as carrier wave in RDS, and TV applications, radio electronic computers and devices to mention but few.

Sinusoidal Oscillations

A transistor can work as an oscillator to produce continuous undamped oscillations of desired frequency if frequency-determining and feedback circuit are properly connected to it. The major difference between these oscillators lie in

- (i) the frequency determining elements ($L-C$ or $R-C$ combination)
- (ii) method of providing positive feedback.


$L-C$ Tank Oscillators or Tuned Oscillators

They can be either Tuned Collector, tuned base, Hartley or Colpitts - a clip.

Tuned Collector Oscillators

The diagram below shows the circuit of Tuned Collector oscillator. It contains tuned L_1-C_1 in the collector and hence the name. The feedback coil L_2 in the base circuit is magnetically coupled to the tank circuit coil L_1 . In practice, L_1 and L_2 form the primary and secondary of the transformer. The biasing is provided by potential divider arrangement. The capacitor C connected in the base circuit provides bias resistance path to the oscillators.

(4)

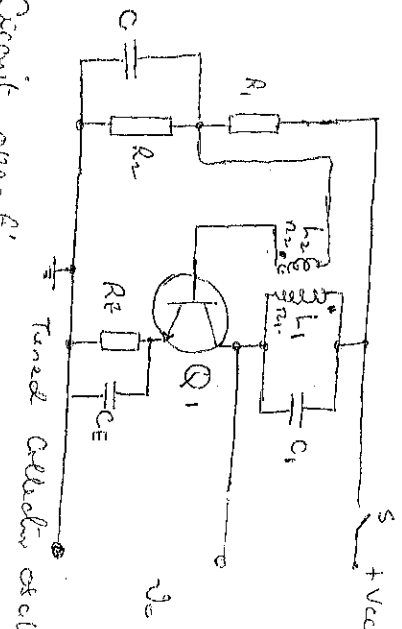

Circuit operation

When switch S is closed, the collector current starts increasing and charges the capacitor C. When fully charged it discharges through coil L₁, setting up oscillations of frequency given by

$$f_o = \frac{1}{2\pi\sqrt{L_1 C_1}}$$

The oscillations induce some voltage in the coil L₂ by mutual induction. The frequency of voltage in the coil L₂ is the same as turns of L₁ and coupling between L₁ and L₂. The voltage across L₂ is opposed between base and emitter and appears in the applied form in the collector circuit, thus overcoming the losses occurring in the tank circuit. The number of turns of L₂ and coupling between L₁ and L₂ are so adjusted that oscillations across L₂ are amplified to a level just sufficient to supply losses to the tank circuit. It is worth mentioning that energy supplied to the tank circuit is in phase with generated oscillations since a phase shift of 180° is caused between voltages L₁ and L₂. A further phase shift of 180° takes place between base-emitter and collector circuit due to transistor properties.

Frequency operation

At resonant frequency f_o , it is known that the inductive reactance = Capacitive reactance i.e.

$$X_L = X_C$$

$$2\pi f_o L_1 = \frac{1}{2\pi f_o C_1}$$

$$4\pi^2 f_o^2 L_1 C_1 = 1$$

$$f_o^2 = \frac{1}{4\pi^2 L_1 C_1}$$

$$\therefore f_o (\text{Hz}) = \frac{1}{\sqrt{4\pi^2 L_1 C_1}} = \frac{1}{2\pi\sqrt{L_1 C_1}}$$

(Point to note is $\frac{1}{\sqrt{L_1 C_1}}$)

the feedback factor, β_v is (5)

$$\beta_v = \frac{n_2}{n_1}$$

for Barkhausen Criterion,

$$A_v \beta_v = 1$$


$$\text{i.e. } \frac{n_2}{n_1} A_v = 1$$

$$A_v = \frac{n_1}{n_2}$$

$\therefore A_v \geq \frac{n_1}{n_2}$ for oscillation to start.

Tuned Base Oscillator

It's is given below:

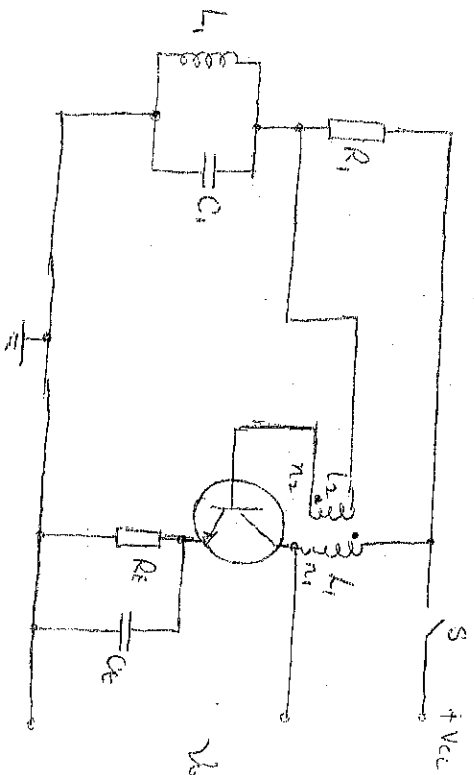

Tuned base oscillator

At resonance frequency f

$$\omega_c L_1 = \frac{1}{\omega_c C_1}$$

$$\omega_c^2 L_1 C_1 = 1$$

$$\omega_c^2 =$$


$$\frac{1}{L_1 C_1}$$

$$(2\pi f_0)^2 = \frac{1}{L_1 C_1}$$

$$\therefore f_0 = \frac{1}{2\pi\sqrt{L_1 C_1}}$$

Hartley Oscillator

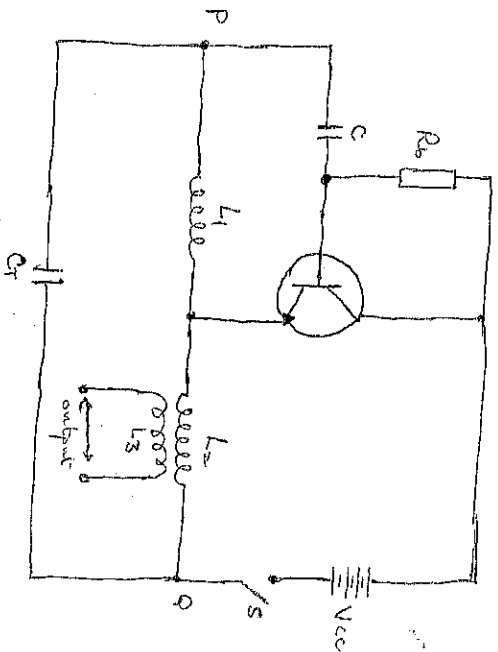This oscillator is very popular in applications where substantial ac or frequency power is needed as in radio transmitters, induction heating and remote control systems. Below is the diagram of Hartley oscillator.



The LC circuit is made up of L_1 , L_2 and C . The coil L_1 is inductively coupled to coil L_2 the combination functions as an auto-transformer. The resistance R_b between collector and base provides the necessary biasing. The capacitor C blocks the dc component. The frequency of oscillation is given by

$$f_o = \frac{1}{2\pi\sqrt{C(L_1+L_2)}}$$

Circuit operation.


When switch S is closed, the collector current starts rising and charges the capacitor C . When it is fully charged, it discharges through coil L_1 and L_2 , setting up oscillations of frequency determined by the above formula. The oscillations across L_1 are applied to the base emitter junction and appear in the amplified form in the collector circuit. The coil L_2 couples the collector circuit energy back into the tank by means of mutual inductance between L_1 and L_2 . In this way energy is being continuously supplied to the LC circuit to overcome the losses occurring in it. It may be seen that this energy

(6)

Suppose to the tank circuit is of correct phase. The inductance P and Q of the auto-transformer $L_1 - L_2$ are 180° out of phase. A further phase-shift of 180° produced by base and collector circuit of the transistor. In this way, every feedback to the tank circuit is in phase with the generated oscillations.

Colpitts Oscillator

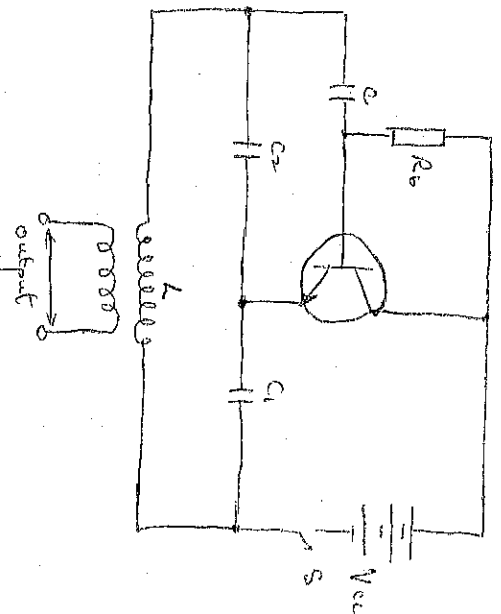The Colpitts oscillator is similar to Hartley oscillator with minor modifications. Whereas Hartley oscillator uses two coils and a capacitor for frequency selection, Colpitts oscillator uses two capacitors and a coil as shown below.



The tank circuit is made up of C_1 , C_2 and L . The frequency of the oscillation is determined by the values of C_1 , C_2 and L and is given by

$$f = \frac{1}{2\pi\sqrt{LC_T}}$$


$$\text{where } C_T = \frac{C_1 C_2}{C_1 + C_2}$$

Circuit operation: When switch S is closed, the capacitors C_1 and C_2 are charged. These capacitors are discharged through coil L setting up oscillations determined by the above equation. The oscillations across C_2 are applied to the base-emitter junction and will appear in the amplified form in the collector circuit and supply power to the tank circuit. Its amount of feedback depends upon the inductive

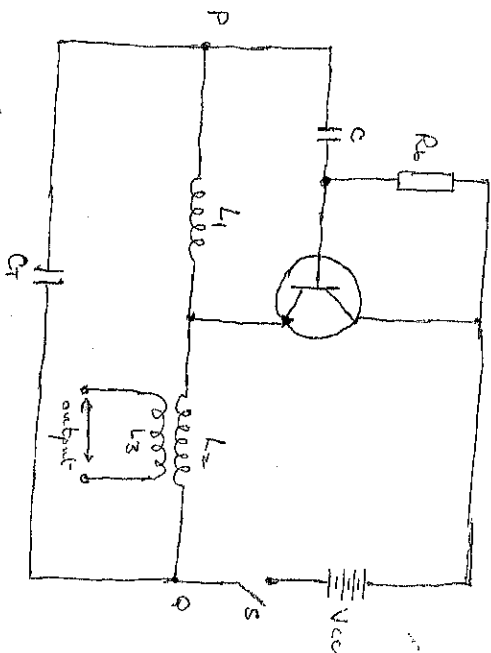(7)

Hartley Oscillator

This oscillator is very popular in applications where substantial radio frequency power is needed as in radio transmitters, induction heating and remote control systems. Below is the diagram of Hartley oscillator.



The tank circuit is made up of L_1 , L_2 and C . The coil L_1 is inductively coupled to coil L_2 the combination functioning as an auto-transformer. The resistance R_b between collector and base provides the necessary biasing. The capacitor C blocks the dc component. The frequency of oscillation is given by

$$f_o = \frac{1}{2\pi\sqrt{C(L_1+L_2)}}$$

Circuit operation:

When switch S is closed, the collector current starts rising and charges the capacitor C . When it is fully charged, it discharges through coil L_1 and L_2 , setting up oscillations of frequency determined by the above formula. The oscillations across L_1 are applied to the base emitter junction and appear in the output from in the collector circuit. The coil L_2 couples the collector circuit energy back into the tank by means of mutual inductance between L_1 and L_2 . In this way energy is being continuously supplied to the tank circuit to overcome the losses occurring in it. It may be seen that the energy

(6)

Capacitors C_1 and C_2 . The smaller the capacitance C_1 , the greater the bandwidth. The capacitors C_1 and C_2 act as a simple alternating voltage divider. Therefore, points P and Q are 180° out of phase. A further phase shift of 180° is produced by the transistor. In this way, feedback is perfectly phased to produce continuous undamped oscillations.

R-C phase shift Oscillator


These oscillators are used as signal generators from lowest audio range up to around 10 MHz. Below, a circuit of phase shift oscillator, it consists of a conventional single transistor amplifier and a RC phase shift network. The phase shift network consists of three sections R_1C_1 , R_2C_2 , and R_3C_3 . At some frequency f_0 , the phase shift produced by each section is 60° so that total phase shift produced by the network is 180° . The frequency of oscillations is given by

$$f_0 = \frac{1}{2\pi RC\sqrt{6}}$$

$$\text{where } R_1 = R_2 = R_3 = R$$

$$C_1 = C_2 = C_3 = C$$

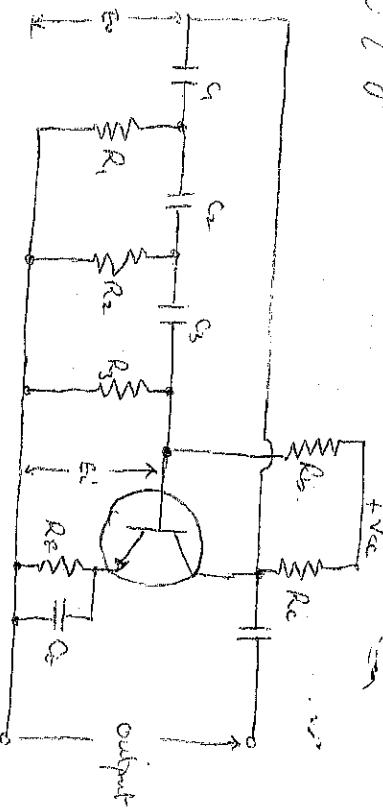Because the opacitive reaction of the network changes at different frequencies, 180° phase shift required occurs only at one frequency.



Circuit operation When the circuit is switched on, it produces oscillations & frequency determined by the formula given above. The output V_o & the amplifier's loadline is RC feedback network. This network produces phase shift of 180° and a voltage V_i appears at its output which is applied to the amplifier's input. The amplifier with correct phase shift of 180° produces by the feedback amplifier. A further phase shift of 180° is produced by the RC network. As a result, the phase shift around the entire loop is 360° i.e. feedback is positive.

Advantages

- It does not require transformers or inductors
- It can be used to produce very low frequencies
- The circuit provides good frequency stability.

Disadvantages

- It is difficult for the circuit to start oscillation
- The circuit gives small output.

Circuit Analysis

It can be seen that the voltage gain & the amplifier $A_v = \frac{V_o}{V_i} = - \left(\frac{5}{\omega^2 R^2 C^2} - 1 \right) - j \left(\frac{6}{\omega RC} - \frac{1}{\omega^3 R^3 C^3} \right) \dots \dots \dots (1)$

Since the second term in the bracket is zero, must be zero at frequency of oscillation, f_o , the gain expression V_o/V_i becomes

$$\frac{V_o}{V_i} = - \left(\frac{5}{\omega^2 R^2 C^2} - 1 \right) \dots \dots \dots (2)$$

The second term is zero (1) can be used to solve for f_o , i.e. $\frac{6}{\omega_o RC} - \frac{1}{\omega_o^3 R^3 C^3} = 0 \dots \dots \dots (3)$

$$\frac{6}{\omega_o RC} = \frac{1}{\omega_o^3 R^3 C^3}$$

$$\omega_o^3 R^3 C^3 \cdot 6 = \omega_o RC$$

(3)

$$\omega_c^2 = \frac{Rc}{R^3 C^3 \times 6}$$

$$\omega_c^2 = \frac{1}{6 R^2 C^2}$$

$$\omega_c = \frac{1}{\sqrt{6} R C} \quad \dots \dots \textcircled{4}$$

$$\therefore f_c = \frac{1}{2\pi \sqrt{6} R C} \quad \text{Hertz} \quad \dots \dots \textcircled{5}$$

At oscillation frequency

$$\frac{V_o}{V_i} = - \left(\frac{5}{\omega_c^2 R^2 C^2} - 1 \right)$$

Substituting for ω_c

$$= - \left(\frac{5}{(1/6 R^2 C^2) R^2 C^2} - 1 \right)$$

$$= - \left(\frac{5(6 R^2 C^2)}{R^2 C^2} - 1 \right)$$

$$= - (30 - 1)$$

$$= -29$$


$$\text{Since } A_v/B_v = 1$$

$$B_v = - \frac{1}{29} \quad \therefore \text{for sustainable oscillations } A_v = -29$$

i.e. slightly higher. i.e. $A_v \geq -29$

WIEN BRIDGE OSCILLATOR

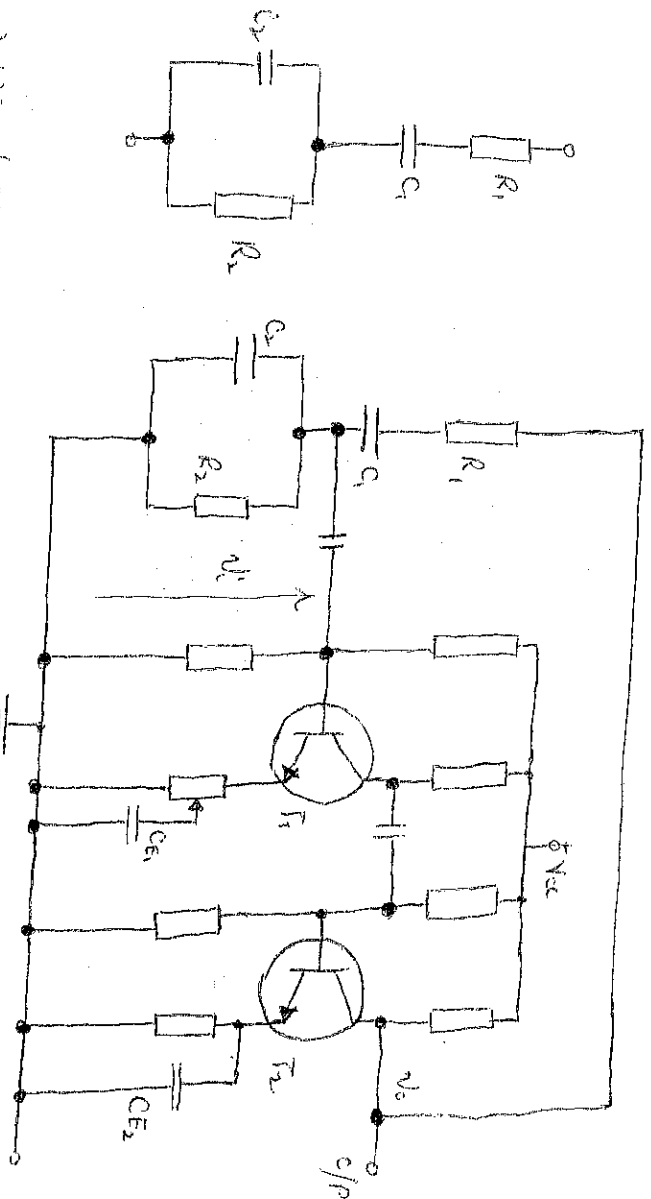This is a standard oscillation circuit for all low frequencies in the range of 10Hz to about 1MHz. It's the most frequently used type of audio oscillator as the output is free from harmonic distortions and ambient temperature. The circuit is given as below:-



(b) Wien-bridge Oscillator

Like phase-shift, the RC circuit is used as the frequency selective network; however, the RC Wien bridge's operation is quite different. The Wien-bridge oscillator uses either a two-stage amplifier or an operational amplifier while the other transistor T_2 serves as an oscillator and provides a phase shift of 180° . The circuit uses positive and negative feedbacks. The positive feedback is through R_1, C_1, R_2, C_2 to the transistor T_1 . The negative feedback is through R_1, C_1, R_2, C_2 to the input of transistor T_1 and T_2 respectively. At the beginning of operation, the reactive load produces a phase lead and phase lag voltage. As the bridge provides a voltage divider, and so, the fraction output voltage feedback through the divider to the first transistor T_1 is given by

$$\beta_r = \frac{R(j\frac{1}{\omega C}) / (R - j\frac{1}{\omega C})}{(R - j\frac{1}{\omega C}) + [R(j\frac{1}{\omega C}) / (R - j\frac{1}{\omega C})]} \quad \text{--- (1)}$$

558
2
11
2/2

Reaction ①

$$\frac{(R-j\omega C)/(R-j\omega C)}{(R-j\omega C) + [(R-j\omega C)/(R-j\omega C)]} \times (R-j\omega C)$$

$$\frac{R\left(\frac{1}{13}\right)}{(R-13)^2} = 430$$

$$\frac{R^2 - \frac{1}{2} R^2 + \frac{1}{2} R^2}{R^2 - \frac{1}{2} R^2 + \frac{1}{2} R^2} = 1$$

$$\frac{R^2 - 3 \frac{R}{2c} + \frac{1}{3c^2}}{1} \quad \times$$

$$\frac{-j^2 R/\omega}{jR^2 - 3j^2 R/\omega - j\frac{1}{\omega C}}$$

$$\frac{R/\nu c}{3R/\nu c + j(R^2 - 1/\omega^2 c^2)} \quad (2)$$

At beginning of operation, for the j term becomes zero as reactive part but only real part $i (R^2 - 1/3 \omega_c^2) = 0$

$$a^2 b^2 = \frac{R / 50^\circ\text{C}}{3R / 120^\circ\text{C}} = \frac{1}{3}$$

Now asking for
for using machine; then of 2nd yield

$$\frac{1}{2} \frac{d^2}{dt^2} \left(\frac{1}{2} \right) = 0$$

$$R^2 = \frac{1}{w^2 c^2}$$

Cher,

$$\frac{1}{R^2 C^2} = \omega_0^2$$

$$f_0 = \frac{1}{2\pi RC} = 31.25 \text{ Hz}$$

It can be deduced from eqn. (3) that for the regime

22

10/11/19

2
1
~~2~~
2
1
1
1

The two transistors T_1 and T_2 must give overall gain of at least 3. Since T_2 is just to give only phase inversion, T_1 can be arranged to give amplification of 1 (i.e. unity gain) and $(G_T = G_1 \times G_2 = 3 \times 1 = 3)$ hence the need for gain adjustment on T_1 and feedbacks on both T_1 and T_2 .

Advantages: It gives constant output, the circuit works quite easily, the overall gain is high because of the transistors and the frequency of oscillation can be changed easily by using a potentiometer.

Disadvantages: The circuit requires 2 transistors and large number of components and it cannot generate very high frequencies (V_{HF}).

At frequency of operation, f_o , the j term becomes zero, i.e. no reactive part but only real part is $(R^2 - \omega_o^2 C^2) = 0$

$$\text{i.e. } f_o = \frac{R/\omega_o C}{3R/\omega_o C} = \frac{1}{3} \quad \dots\dots\dots (3)$$

Now solving for f_o using negative j term of eqn (2) yields

$$R^2 - \omega_o^2 C^2 = 0$$

$$R^2 = \frac{1}{\omega_o^2 C^2}$$

Therefore,

$$\omega_o^2 = \frac{1}{R^2 C^2}$$

$$f_o = \frac{1}{2\pi RC} \quad \text{or } f_3$$

It can be deduced from eqn (3) that for the magnitude of A_v for sustainable oscillation is given from

$$A_v/A_v = 1$$

$$A_v \cdot \frac{1}{3} = 1$$

$$\therefore A_v \geq 3$$

The two transistors T_1 and T_2 must give overall gain of at least 3. Since T_2 is just to give only phase inversion, it can be arranged to give amplification of 1 (i.e. unity gain) and T_1 can be arranged to give amplification of 3 or more (overall gain $A_v = G_1 \times G_2 = 3 \times 1 = 3$) hence the need for gain adjustment on T_1 and feedbacks on both T_1 and T_2 .

Advantages: It gives constant output, the circuit works quite easily, the overall gain is high because of two transistors and the frequency of oscillation can be changed readily by using a potentiometer.
Disadvantages: The circuit requires 2 transistors and large number of components and it cannot generate very high frequencies (VHF).

Limitations of ΔC and ΔR oscillators


The ΔC and ΔR discussed earlier have their own limitations. The major problem is such circuit is that their frequency of operation does not remain strictly constant. It is because the values of resistors and inductors which are the frequency determining elements in these circuits change with temperature. This causes the change in the frequency of the oscillator. However in many applications it is desirable and necessary to maintain the frequency constant with extreme low tolerances. For example, it is desired that frequency of the broadcasting station should not change due to change in temperature or any other reason or else listeners will not be tuning their radios for any particular station.

Solution.

In order to maintain constant frequency, piezoelectric crystals are used in place of ΔC or ΔR . Circuits as temperature effect on the crystals is very minimal. Oscillators of this type are called CRYSTAL OSCILLATORS. For less serious work, ΔC and ΔR can be used with i) provide frequency determining network, with low tolerance components ii) provide feedback to compensate the effect of temperature.

TUTORIALS

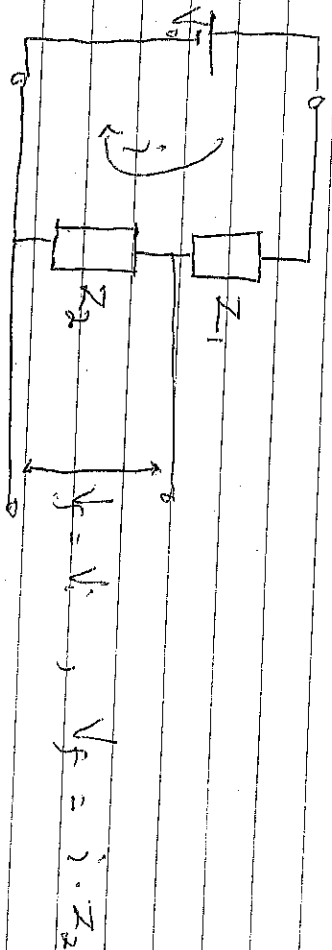$V_s = V_f \Rightarrow$ WILEY BRIDGE OSCILLATOR



$$i = \frac{V_s}{Z_1 + Z_2} \quad \therefore V_f = \frac{V_s \cdot Z_2}{Z_1 + Z_2}$$

$$R = \frac{V_f}{V_s} = \frac{Z_2}{Z_1 + Z_2}$$

$$Z_2 = \frac{R}{\cancel{j\omega C} \times \cancel{1 + j\omega C}} = \frac{1 + j\omega C}{j\omega C}$$

$$Z_1 = R + \frac{1}{j\omega C}$$

$$Z_2 = \frac{j\omega R}{j\omega C + j^2\omega^2 R} = \frac{1 + j\omega R}{j\omega C}$$

$$Z_1 = \frac{j\omega R C + 1}{j\omega C}$$

$$Z_2 = \frac{j\omega R}{j\omega C + j^2\omega^2 R}$$

$$Z_1 = \frac{1 + j\omega R C}{j\omega C}$$

$$\frac{V_f}{V_s} = \frac{R}{1 + j\omega R C} \times \frac{j\omega R}{j\omega C + j^2\omega^2 R}$$

$$Z_2 = R \cdot \frac{1}{j\omega C}$$

$$R + \frac{1}{j\omega C}$$

$$= \frac{R}{(1 + j\omega R C) + R}$$

$$Z_2 = \frac{R}{j\omega C}$$

$$= \frac{R}{(1 + j\omega R C)^2 + j\omega R C}$$

(1)

$$= \frac{j\omega C}{1 + j\omega R C + j\omega^2 R^2 C + j\omega R C} = \frac{j\omega C}{1 + 3j\omega R C - \omega^2 R^2 C^2}$$

$$\frac{V_f}{V_o} = \frac{j\omega R C}{1 - \omega^2 R^2 C^2 + 3j\omega R C} \cdot \frac{j}{j}$$

$$= \frac{-\omega R C}{1 - \omega^2 R^2 C^2 + 3j\omega R C}$$

$$j - j\omega^2 R^2 C^2 - 3\omega R C$$

$$= \frac{\omega R C}{-j + j\omega^2 R^2 C^2 + 3\omega R C}$$

$$\frac{V_f}{V_o} = \frac{\omega R C}{3\omega R C - j(1 - \omega^2 R^2 C^2)}$$

$$1 - \omega^2 R^2 C^2 = 0$$

$$\omega^2 R^2 C^2 = 1$$

$$\omega^2 = \frac{1}{R^2 C^2}$$

$$\omega = \frac{1}{RC}$$

$$f = \frac{1}{2\pi RC}$$


$$\frac{V_f}{V_o} = K = \frac{\omega R C}{3\omega R C} = \frac{1}{3}$$

$$AK = 1$$

$$\frac{1}{3} A = 1$$

$$A \geq 3$$

2

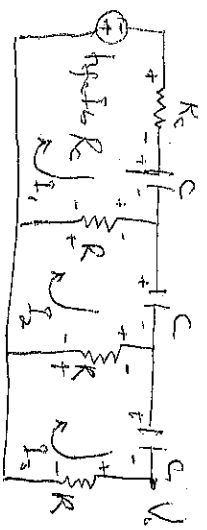

KVL to loop ①, ②, ③

loop ①

$$-h_{fe} I_{b2} R_c - I_1 R_c - I_1 \cdot \frac{1}{j\omega C} - I_1 R + I_2 R = 0$$

$$h_{fe} I_{b2} R_c + I_1 R_c + I_1 \cdot \frac{1}{j\omega C} + I_1 R - I_2 R = 0$$

$$I_1 \left[R + R_c + \frac{1}{j\omega C} \right] - I_2 R + h_{fe} I_{b2} R_c = 0$$

$$\text{Since } I_{b2} = I_3$$

$$I_1 \left[R + R_c + \frac{1}{j\omega C} \right] - I_2 R + I_3 h_{fe} R_c = 0$$

$$\text{Loop ②} \quad -R \left(2R + \frac{1}{j\omega C} \right) + h_{fe} R^2 R_c = 0$$

$$-I_2 \cdot \frac{1}{j\omega C} - I_2 R + I_3 R - I_2 R + I_1 R = 0$$

$$-I_2 \cdot \frac{1}{j\omega C} - 2I_2 R + I_1 R + I_3 R = 0$$

$$-I_1 R + I_2 \left[2R + \frac{1}{j\omega C} \right] - I_3 R = 0$$

loop ③

$$-I_3 \cdot \frac{1}{j\omega C} - I_3 R - I_3 R + I_2 R = 0$$

$$-I_3 \cdot \frac{1}{j\omega C} - 2I_3 R - I_2 R = 0$$

$$-I_2 R + I_3 \left[2R + \frac{1}{j\omega C} \right] = 0$$

③

$$\begin{aligned} & \frac{3R^3}{\omega^2 C^2} - \frac{4R^2}{\omega^2 C^2} + \frac{4R^2}{j\omega C} + \frac{3R^2 R_c}{\omega^2 C^2} \\ & + \frac{4R R_c}{j\omega C} + \frac{3R^2}{j\omega C} - \frac{1}{j\omega^3 C^3} + \frac{4R}{j\omega^3 C^3} \end{aligned}$$

①

②

$$\begin{bmatrix} R + R_c + \frac{1}{j\omega C} & -R & h_{fe} R_c \\ -R & 2R + \frac{1}{j\omega C} & -R \\ 0 & -R & 2R + \frac{1}{j\omega C} \end{bmatrix} = 0$$

$$\begin{aligned} & + R \left\{ -R \left(2R + \frac{1}{j\omega C} \right) - 0 \right\} + h_{fe} R_c (R^2 - 0) \\ & \left[R + R_c + \frac{1}{j\omega C} \right] \left\{ 4R^2 + \frac{2R}{j\omega C} + \frac{2R}{j\omega C} + \frac{1}{j^2 \omega^2 C^2} - R^2 \right\} \end{aligned}$$

$$\left[R + R_c + \frac{1}{j\omega C} \right] \left\{ 4R^2 - R^2 - \frac{1}{\omega^2 C^2} + \frac{4R}{j\omega C} \right\}$$

$$\text{Loop ②} \quad \left[R + R_c + \frac{1}{j\omega C} \right] \left\{ 3R^2 - \frac{1}{\omega^2 C^2} + \frac{4R}{j\omega C} \right\}$$

$$\left[R + R_c \right] \left[3R^2 - \frac{1}{\omega^2 C^2} \right] + \frac{1}{j\omega C} \left[3R^2 + \frac{4R}{\omega^2 C^2} \right]$$

$$\left[R + R_c + \frac{1}{j\omega C} \right] \left[3R^2 + \frac{4R}{j\omega C} - \frac{1}{\omega^2 C^2} \right] - R^3 \left[2R + \frac{1}{j\omega C} \right] + h_{fe} R^2 R_c = 0$$

$$3R^3 + \frac{4R^2}{j\omega C} - \frac{R^2}{\omega^2 C^2} + 3R^2 R_c + \frac{4R R_c}{j\omega C} + \frac{4R^2}{\omega^2 C^2} + \frac{3R^3}{j\omega C} - \frac{1}{j\omega^3 C^3} - \frac{2R^3}{j\omega C} + h_{fe} R^2 R_c = 0$$

$$R^3 + \frac{4R^2}{j\omega C} + \frac{3R^2}{j\omega C} - \frac{R^2}{\omega^2 C^2} - \frac{R^2}{\omega^2 C^2} + \frac{4R R_c}{j\omega C} + 3R^2 R_c - \frac{R^2}{\omega^2 C^2} + \frac{4R R_c}{j\omega C} + h_{fe} R^2 R_c = 0$$

$$R^3 + \frac{6R^2}{j\omega C} - \frac{5R}{\omega^2 C^2} - \frac{R_c}{\omega^2 C^2} + 3R^2 R_c + \frac{4R R_c}{j\omega C} + h_{fe} R^2 R_c = 0$$

$$R^3 + 3R^2 R_c - \frac{1}{\omega^2 C^2} [5R + R_c] + h_{fe} R^2 R_c + \frac{6R^2}{j\omega C} + \frac{4R R_c}{j\omega C} - \frac{1}{j\omega^3 C^3} = 0$$

$$R^3 + 3R^2 R_c - \frac{1}{\omega^2 C^2} (5R + R_c) + h_{fe} R^2 R_c - j \left[\frac{6R^2}{\omega C} - \frac{4R R_c}{\omega C} + \frac{1}{\omega^3 C^3} \right] = 0$$

$$R^3 + 3R^2 R_c - \frac{1}{\omega^2 C^2} (5R + R_c) + h_{fe} R^2 R_c - j \left[\frac{6R^2}{\omega C} + \frac{4R R_c}{\omega C} - \frac{1}{\omega^3 C^3} \right] = 0$$

for oscillation

$$\frac{6R^2}{\omega C} + \frac{4R R_c}{\omega C} - \frac{1}{\omega^3 C^3} = 0 \quad \text{multiply } \omega C \text{ to both side}$$

$$6R^2 + 4R R_c - \frac{1}{\omega^2 C^2} = 0$$

$$6R^2 + 4R R_c = \frac{1}{\omega^2 C^2} \quad \text{--- (4)}$$

$$\omega^2 = \frac{1}{C^2 (6R^2 + 4R R_c)} \quad \text{but } R = \frac{R_c}{R} \text{ and } R_c = R_c$$

$$\omega^2 = \frac{1}{C^2 (6R^2 + 4R(R_c))}$$

$$\omega^2 = \frac{1}{C^2 (6R^2 + 4R^2 R_c)}$$

$$\omega^2 = \frac{1}{C^2 R^2 (6 + 4R_c)}$$

$$\omega = \frac{1}{RC \sqrt{6 + 4R_c}} \quad \text{or } f = \frac{1}{2\pi RC \sqrt{6 + 4R_c}}$$

(3)

$$R^3 + 3R^2 R_c - (5R^2 + 4R R_c)(5R + R_c) + h_{fe} R^2 R_c = 0 \quad (P.1.2)$$

$$R^3 + 3R^2 R_c - 30R^3 - 56R^2 R_c - 20R^2 R_c - 4RR_c^2 +$$

$$h_{fe} R^2 R_c = 0$$

$$-29R^3 - 23R^2 R_c - 4RR_c^2 + h_{fe} R^3 R_c = 0$$

$$h_{fe} R^3 R_c = 29R^3 + 23R^2 R_c + 4RR_c^2$$

$$h_{fe} = \frac{29R^3}{R^2 R_c} + \frac{23R^2 R_c}{R^2 R_c} + \frac{4RR_c^2}{R^2 R_c}$$

$$h_{fe} = \frac{29R}{R_c} + 23 + \frac{4R_c}{R}$$

$$k = \frac{R_c}{R} \quad k^{-1} = \frac{R}{R_c}$$

$$h_{fe} = \frac{29}{k} + 23 + 4k$$

$$h_{fe}(k) = 29 + 2k + 4k^2 \quad |c = 0$$

$$\frac{dh_{fe}}{dk} = 0$$

$$h_{fe(k)} = 29$$

$$-\frac{29}{k^2} + 0 + 4 = 0$$

$$-\frac{29}{k^2} = -4$$

$$k^2 = \frac{29}{4} \Rightarrow k = \sqrt{\frac{29}{4}} = 2.6925$$

(4)

$$h_{fc(\min)} A \geq 44.5$$

when $R_c = 0$

$$A = \frac{V_o}{V_{in}} = - \left(\frac{5}{W^2 R^2 C^2} - 1 \right) - j \left(\frac{6}{WR_c} - \frac{1}{W^3 R^3 C^3} \right)$$

at Resonance freq. imaginary part is equal to zero, then the gain becomes

$$\frac{V_o}{V_{in}} = - \left(\frac{5}{W^2 R^2 C^2} - 1 \right) = 0 \quad \text{--- (1)}$$

first, if operation

$$\frac{6}{WR_c} - \frac{1}{W^3 R^3 C^3} = 0 \quad \xrightarrow{\text{--- (2)}} \quad \frac{6}{WR_c} = \frac{1}{W^3 R^3 C^3}$$

$$6 = \frac{1}{W^3 R^2 C^3}$$

$$W^3 = \frac{1}{R^2 C^3 6}$$

$$W = \frac{1}{RC \sqrt[3]{6}}$$

$$f = \frac{1}{2\pi RC \sqrt[3]{6}}$$

The gain can be obtained as

$$- \left(\frac{5}{(\frac{1}{RC \sqrt[3]{6}})^2 R^2 C^2} - 1 \right) = A$$

$$- \left(\frac{5}{1/6} - 1 \right) = A$$

$$\begin{aligned} - (5 \times 6 - 1) &= A \\ - (30 - 1) &= A \\ - 30 + 1 &= A \\ - 29 &= A \\ A &\geq -29 \end{aligned}$$

$$A_v A_v = 1$$

$$- 29 A_v = 1$$

$$A_v = -\frac{1}{29}$$

(5)

(2)

$$f = \frac{1}{2\pi \sqrt{LC}}$$

$$\text{where } C = \frac{C_1 C_2}{C_1 + C_2}$$

$$B = \frac{C_2}{C_1} \quad \text{and} \quad A = \frac{C_1}{C_2}$$

for sustainable oscillation the loop gain

$$AB = 1$$

phase 60° of oscillation give sinusoidal waveform

Multivibrator


There are three types of multivibrators called Astable, Bistable and monostable. These circuits give square wave unlike Hartley or Colpitts oscillators.

Astable This is the circuit that oscillates between two states, HIGH and LOW without any external trigger. Bistable: This is the circuit that may be in any one of the two states indefinitely. It can only switch state to another stable state given an external trigger. Monostable is the one which is stable in only one state.

It triggered it goes into unstable state briefly depending upon the timing components before reverting to the stable state.

~~1st~~

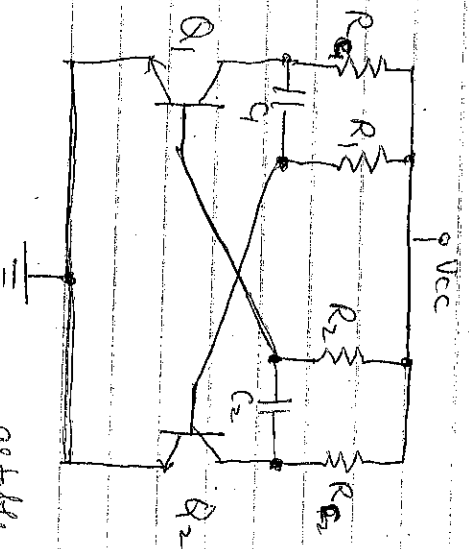Astable multivibrator: Derivation of frequency of operation of the circuit



astable multivibrator circuit

(3)

If $T_1 = 0.69 R_1 C$, high state time constant
 $T_2 = 0.69 R_2 C$, low state time constant
then $T = T_1 + T_2 =$ time period of the circuit

For a 50% duty cycle = $\frac{T_2}{T_1 + T_2}$

$$\frac{50}{100} = \frac{T_2}{T_1 + T_2}$$

$$100 T_2 = 50 T_1 + 50 T_2$$

$$\therefore 50 T_2 = 50 T_1$$

$$T_2 = T_1$$

$$\text{for } T_2 = T_1, \quad R_1 = R_2 = R$$

$$C_1 = C_2 = C$$

$$\therefore T = T_1 + T_2 = 0.69 RC + 0.69 RC$$
$$= 1.38 RC$$

$$\text{But } f = \frac{1}{T} = \frac{1}{1.38 RC}$$

To choose the frequency, keeping the same square-wave space, both RC time constant will be changed together at the same time. But to change both frequency and mark-space ratio, only one RC time constant network need to be changed.

Applications of multivibrators in digital circuits.

- for timing digital circuits (clock)
- for frequency digital circuits
- for synchronization of digital circuits

Example 1. Design an astable multivibrator using transistors given the following specifications:

frequency of operation = 50 kHz

$$V_{BE1} = 0.3V \text{ for transistor } Q_1$$

$$V_{BE2} = 0.3V \text{ for transistor } Q_2$$

$$V_{CE1} = 0.3V \text{ for transistor } Q_1$$

$$V_{CE2} = 0.3V \text{ for transistor } Q_2$$

$$\beta_1 = 100 \text{ for transistor } Q_1$$

$$\beta_2 = 100 \text{ for transistor } Q_2$$

(5)

(4)

$$V_{cc} = 12V$$

$$I_{C1} = 20mA \text{ for } Q_1$$

$$I_{C2} = 20mA \text{ for } Q_2$$

Let R_{C1} and R_{C2} be collector resistances for Q_1 and Q_2

$$\therefore V_{CE1} = V_{cc} - V_{CE1}$$

$$= 12 - 0.3 = 11.7V$$

$$\therefore R_{C1} = \frac{V_{CE1}}{I_{C1}} = \frac{11.7}{20mA} = 585\Omega$$

$$\text{Similarly for } R_{C2} = \frac{V_{CE2}}{I_{C2}} = \frac{11.7}{20mA} = 585\Omega$$

$$\text{For 50\% duty cycle} = \frac{T_2}{T_1 + T_2}$$

$$\frac{50}{100} = \frac{T_2}{T_1 + T_2}$$

$$50T_1 + 50T_2 = 100T_2$$

$$50T_1 = 50T_2$$

$$T_1 = T_2$$

$$\therefore R_1 = R_2 = R$$

$$C_1 = C_2 = C$$

$$\text{Min base Current } I_{Bmin} = \frac{I_C}{\beta}$$

$$\text{but s.t. } I_B = 3 \times I_{Bmin} = 3 \times \frac{I_C}{\beta}$$

$$\therefore R_1 = \frac{V_{cc} - V_{BE1}}{I_{B1}}$$


$$\text{but } I_{B1} = 3 \times \frac{I_{C1}}{\beta_1} = \frac{3 \times 20mA}{100} = 600\mu A$$

$$\therefore R_1 = \frac{12 - 0.3}{600\mu A} = 19.5k\Omega$$

$$\text{Similarly } R_2 = 19.5k\Omega$$

$$\text{from } f = \frac{1}{1.38RC}, \quad C = \frac{1}{1.38 \times 19.5k \times 50kHz} \\ \approx 0.7\mu F$$

(5)

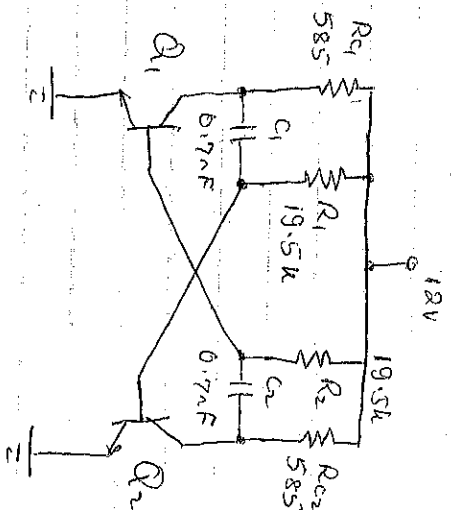

(7)

4) With negative feedback, an amplifier gives an output of 10V with an input of 0.5V. When the feedback is removed, it requires 0.25V input for the same output. Calculate (i) gain without feedback (ii) feedback factor β .

5) Draw the basic negative feedback amplifier which will modify input and output impedances to match microphone and loudspeaker respectively.

(7)


- a) Draw an amplifier block diagram and show that
 b) Show that $A_{VF} = \frac{A}{1+A\beta}$
 c) If the open loop $A = 10^5$ and the feedback factor $\beta = 5 \times 10^{-5}$, find the gain with feedback.

- d) If the original β of an amplifier is 12 what must be the feedback factor to achieve a closed loop gain of 8.

$$\beta = \frac{k_1}{k_2} \text{ and } A = \frac{k_2}{k_1}$$

~~Q4.~~

Coupled Oscillator

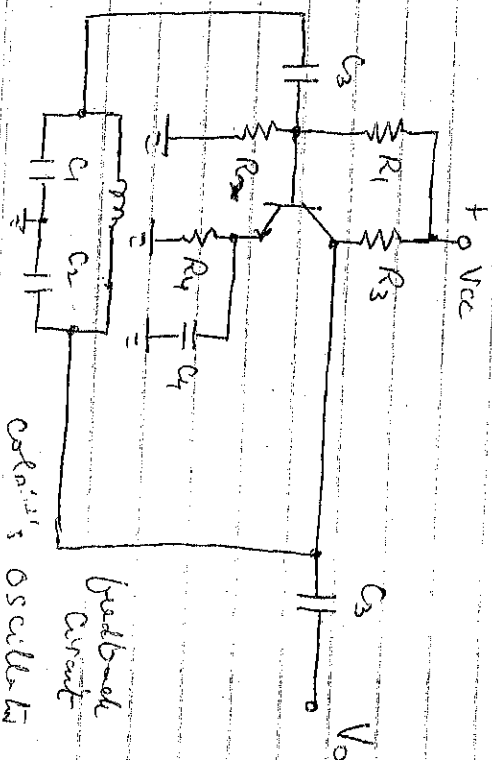

Coupled Oscillator
 Feedback Circuit