

LESSON Note

ON

(EEE 437)

Electronic

Drafting & DESIGN

GOAL:

The Course is designed to provide the student with knowledge and skill in design & drafting of electronic circuits.

OBJECTIVES:

- 1- Know / Identify the symbols of components used in electronics
- 2- Know how to draw Schematic diagrams
- 3- Know how to draw block & logic diagrams
- 4- Know Construction of a dependable & easy-to-troubleshoot prototype or modification set.
- 5- Know the Production of Prints Circuit boards
- 6- Know how to draw Wiring Assembly Diagrams
- 7- Understand the Various types of design & layout of Communication Systems.

MEANING OF BOTH DESIGN & DRAFTING

- DESIGN: This is simply the underlying planning that lays the basis for the making of every device or a system. The person designing is called a DESIGNER. Designing often requires a designer to consider the aesthetic, functional and other aspects of an object or a process, which usually requires considerable research, thought, modelling, interactive adjustment and re-design.

DRAFTING: Is the Process of producing engineering drawing and the skill of producing them is often referred to as technical drawing or drafting. ^{which} Design & drafting can not be done by anyone not familiar with all the Electronics Code & standards needed for the design.

1.0 → Commonly Used Electronic Symbols

1.1 WIRES AND CONNECTIONS:

COMPONENT

- WIRE




Circuit Symbol

function

- To pass current very easily from one part of a circuit to another.

- WIRES JOINED

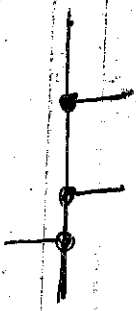

- A 'blob' should be drawn where wires are connected (joined), but it is sometimes omitted, wired connected at

Crossroads should be staggered slightly to form 2+ junctions, i.e. as shown on the right.

- WIRES NOT JOINED



In complex diagrams it is often necessary to

draw wires crossing even though they are not connected. It is preferred the 'bridge' symbol shown on the right because the simple crossing on the left may be misread as a join where you have forgotten to add a blob.

POWER SUPPLIES:

COMPONENT

- CELL



Circuit Symbol

function

- If supplies electrical energy. The larger terminal (on the left) is

positive (+). A single cell is often called a battery, but strictly a battery is two or more cells joined together.

- BATTERY



- Supplies electrical energy. A battery is more than one cell.

The larger terminal (on the left) acts as the

- DC Supply




Supplies electrical energy


DC = Direct Current, always flowing in the direction

Component Circuit Symbol Functions

- AC Supply  Supplies electrical energy.
 AC = Alternating Current, Continually changing direction.

- FUSE  This is a safety device which will 'blow' (melt) if the current flows in it. it exceeds a specified value.

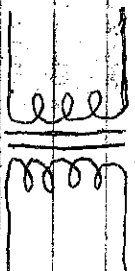- TRANSFORMER  Two coils of wire linked by an iron core. Transformers are used to step-up (increase) and step-down (decrease) AC voltages. Energy is transferred between the coils by the magnetic field in the core. There is no electrical connection b/w the coils.

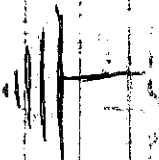- EARTH  This is simply a connection to earth. For many electronic cts this is the 0V (zero-volts) of the

Power Supply, but for mains electricity and some radio circuits it really means the earth is also known as "Ground".

Output Devices Symbols Functions

- LAMP LIGHTING  This is a transducer which converts electrical energy to light. The symbol is used for lamps providing illumination, for example a car headlamp or torch bulb.


- LAMP (Indicator)  A transducer which converts electrical energy to light. This symbol is used for a lamp which is an indicator, for example a warning light on a car dashboard.

- HEATER



This is a transducer which converts electrical energy to heat.

- Motor :

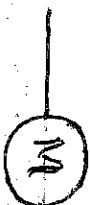

A transducer which converts electrical energy to kinetic energy (motion).

- BELL



This is a transducer which converts electrical energy to sound.

- BUZZER



A transducer which converts electrical energy to sound.

- Inductor

(COIL, SOLENOID)



A coil of wire which creates a magnetic field when current passes through it. It may have an iron core inside the coil. It can be used as a transducer converting electrical energy to mechanical energy by pulling on something.

- Switches :


Component

Circuit Symbol

Functions

- Push Switch

(Push-to-make)

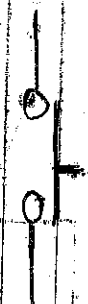


A push switch allows current to flow only when the button is pressed. This is the switch used to operate a doorbell.

- Push-to-BREAK Switch :



This type of push switch is normally closed (on), it is open (off) only when the button is pressed.

On-off-Switch (SPST)

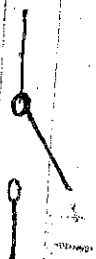


SPST = Single Pole, Single Throw.
An on-off switch allows current to flow only when it is in the closed position.

2-Way-Switch (SPDT)




SPDT = Single Pole, Double Throw.
A 2-way changer switch directs the flow of current to one of two routes according to its position. Some SPDT switches have a central off position and are described as 'on-off-on'.

Dual On-off Switch (DPST)

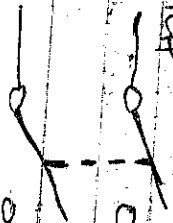


DPST = Double Pole, Single Throw.
A dual on-off switch is often used to switch mains electrical because it can isolate both the live and neutral connections.

REVERSING SWITCH (DPDT)

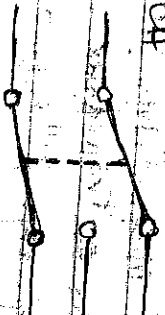

DPDT = Double Pole, Double Throw.
This switch can be wired up as a reversing switch for a motor. Some DPDT switches have a central off position.

RELAY

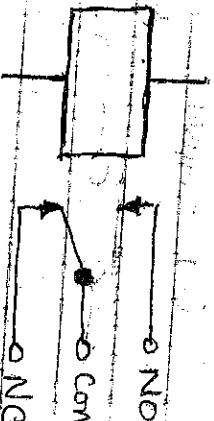

An electrically operated switch, for example a 24V battery can connected to the coil can switch a 230V AC Mains circuit.

N/O,

NO = Normally Open


COM = Common

NC = Normally closed.

Resistors :

COMPONENT

Normal Resistor

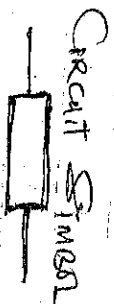

Function

A resistor restricts the flow of current, for example to 1.

Limit the current passing through an LED. A resistor is used with a capacitor in a timing circuit. Some publications still use the old resistor symbol: 

- VARIABLE RESISTOR

(RHEOSTAT)



This type of variable resistor with 2 contacts

to control current. Examples include, adjusting lamp brightness, adjusting motor speed, and adjusting the rate of flow of charge into a capacitor in a timing circuit. A rheostat is usually used.

- VARIABLE RESISTOR

(PRESSET)



This type of variable resistor (preset) is its

operated with a small screwdriver or similar tool. It is designed to be set when the circuit is made & then left without further adjustment. Presets are cheaper than normal variable resistors so they are often used in projects to reduce the cost.

- VARIABLE RESISTOR

(POTENTIOMETER)



This type of variable resistor with 3 contacts

(a potentiometer) is usually used to control voltage. It can be used like this as a transducer converting position (angle of the control spindle) to an electrical signal.

- Ceramic
 - Electrolytic
 - Film
 - Silver mica
 - Polyester
 - Paper
 - Air
 - Variable
 - Fixed
 - Capacitors are divided into two mechanical groups
 - Fixed capacitors with fixed capacitance values & variable
 capacitors with variable (tunable) or adjustable (tunable)
 capacitance values. The most important group is the fixed
 capacitors. About 90% of the capacitors are from the dielectric

A capacitor stores electric charge. A capacitor is used

used as a resistor in a timing circuit. It can also be used as a filter to block DC signals but pass AC signals. - capacitors also have functions to keep the voltage at a certain level

- AC flowing but not DC
- removing noise

A Capacitor stores electric charge. Its Type must be correct.

The correct way round. A capacitor is used with a resistor in a tuning circuit. It can also be used as a full to block DC signals but pass AC signals.

This type of variable capacitor (a trimmer) is operated with a knob. It is used to tune the radio.

Small Screw driver or Similar tool. It is designed to set when the circuit is made and then left with further adjustment.

It is a hard leaved, glaucous, woody, moist
herb. The seeds form a semicircular, moist
layer in the middle. Some are greenish, some brownish.
They are made from a semicircular, moist
layer in the middle. Some are greenish, some brownish.
They are made from a semicircular, moist
layer in the middle. Some are greenish, some brownish.

device which only allows current to flow in one direction -
- using diode
- conduct but not reverse

This is simply a transdiode which converts electrical energy to light.

This is simply a transistor which converts electrical energy to light.

- This is a special diode which is used to maintain a

- A light sensitive diode.

TRANSISTOR:

- TRANSISTOR (NPN)

* An diode AC or DC
- Diodes conduct only when they are forward biased.
Since AC reverses its direction periodically, the diode conducts only in half cycles & insulates during the other half cycles.
- Two properties of a diode is used up rectification of AC into DC.



This is simply a semi-conductor device i.e. able to amplify or rectify an electric current.

It can be used with other components to make an amplifier or switching circuit.

- TRANSISTOR (PNP)




Semi-conductor device & electrically controlled. It has 3 terminals: emitter, base, & collector. It is used to amplify signals. Transistors are broadly divided into three types: (1) Bipolar Junction Transistors (BJT), (2) Field Effect Transistors (FET), (3) Insulated Gate Transistors (IGT).

Field effect transistors (FET) are used to amplify signals. They are used in a variety of applications, including amplifiers, switches, and logic gates.

Insulated Gate Transistors (IGT) are used to amplify signals. They are used in a variety of applications, including amplifiers, switches, and logic gates.

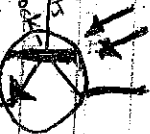Also a semi-conductor device that amplifies current in a circuit. It can be used with other components to produce an amplifier.



This is a light-sensitive transistor. It is used to detect light. It is a type of transistor that is sensitive to light. It is used in a variety of applications, including light detectors, light sensors, and light switches.

Audio & Radio Devices:

- MICROPHONE




- A transducer which converts sound to electrical energy.

- CARPHONE




- A transducer which converts electrical energy to sound.

- LOUDSPEAKER

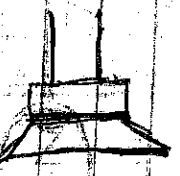

- A transducer which converts electrical energy to sound.

- PIEZO TRANSDUCER

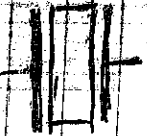

- A transducer which converts electrical energy to sound.

- AERIAL (ANTENNA)



- A device which is designed to receive or transmit radio signals. It is also known as an antenna.

Component

Circuit Symbol

Functions

- AMPLIFIER



An operational amp. is an integrated circuit that behaves like a high-gain difference amp. It amplifies the diff. b/w two input voltages. Op amp. is a triangle that has two inputs & a single output.
An electronic device for increasing the amplitude of electrical signals, used chiefly in sound reproduction.

An amplifier circuit with one input. Really it is a block

diagram symbol because it

represents a circuit rather than just one component.

METERS AND OSCILLOSCOPE:

- OHMMETER



An ohmmeter is used to measure resistance. Most multimeters have an ohmmeter setting.

- AMMETER



An ammeter is used to measure current.

- VOLTMETER



A voltmeter is used to measure voltage. The proper voltage for voltage is 'Potential Difference' but most people prefer voltage.

- GALVANOMETER



A galvanometer is a very sensitive meter which is used to measure tiny currents, usually just or less.

- OSCILLOSCOPE



An oscilloscope is used to display the shape of electrical signals and it can be used to measure their voltage and time period.


SENSORS (INPUT DEVICES):

1 DR =

Light dependent Resistor



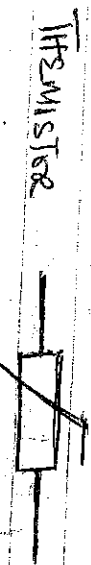A transducer which converts lightness (light) to resistance (an electrical property).



A transducer which converts Temperature (heat) to resistance. Can electrical property.

LOGIC GATES

Basically Logic Gates Process signals which represents True (1, high, +Vs, on) or False (0, low, 0V, off). Logic gate are physical devices that can be used to implement logic functions.

There are two sets of symbols, i.e. traditional and IEC (International Electrotechnical Commission).

Gate Type	Traditional	IEC	function
-----------	-------------	-----	----------

NOT



symbol



symbol

A not gate is also called as inverter. If only have one input. The '0' on the output means 'not'. The output of a NOT gate is the inverse (opposite) of its input. So the output is true when the input is false.

Truth Table $\Rightarrow$

X	$\bar{X}$
1	0
0	1

logical multiplication representation.



These is a logic of with more than one input & usually


Truth Table:

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

No output signal will be produced unless a pulse is applied to all inputs simultaneously. i.e.

Logical multiplication formation: If any of the input are zero, the o/p will also be zero.

- NAND

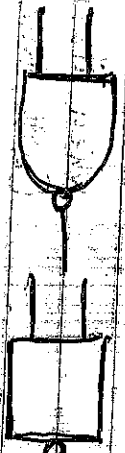

This is a combination of a NOT & AND function. It

Type

TRAD. SYMBOL IEC

FUNCTION

- NAND



It has two or more inputs and one output. The output is logic '0' on the output means 'not' showing that its output is true unless all its inputs are true.

- OR




An OR gate can have two or more inputs. The output of an OR gate is true when at least one of its inputs is true.

- NOR



A NOR gate have two or more inputs. The 0 on the output means 'not' meaning that it is a NOT OR gate. The output of a NOR gate is true when none of its inputs are true.

- EX-OR

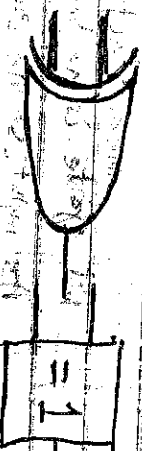

An EX-OR gate only have two inputs. The output of an EX-OR gate is true when its inputs are different (one true, one false).



- EX-NOR



An EX-NOR gate can only have two inputs. The '0' on the output means "not" showing that it is a NOT EX-OR gate. The output of an EX-NOR gate is true when its inputs are the same (both true or both false).

ELECTRONIC COMPONENT IDENTIFICATION & INFORMATION

RESISTORS;

Standard resistors are "not" polarised and can be placed in the PCB any way around.

The most common resistor have four bands.

* Bands 1 and 2 - identify the first two digits, band 3 is the multiplier and band 4 is the tolerance (normally Gold 5%)

The Multipliers are;

$$R \approx \times 0$$

$$K = \times 1,000$$

$$M = \times 1,000,000$$

The Kit Parts list might contain, for example, a 4K7 resistor. The K refers to the number multiplier ($K = \times 1,000$). The position of the K between the 4 and 7 identifies the position of the decimal point so one 'have';

$$4.7 \times 1,000 = 4,700 \text{ Ohms (with a colour code of Yellow, violet, Red)}$$

Another example is say 5GR. This gives us $5G \times 0 = 56 \text{ Ohms}$ resistor with colour code; Green, Blue, Black.

You will find, some five band resistors in our kits and the colour code is likely to be associated with the same precision 1% and 2% types. The work in a similar way to the four band but the first three bands are used to determine the numbers, and band 4 is always the multiplier and band 5 is the tolerance. See the table below for more details;

IDENTIFYING COMPONENTS USING LETTERS

13

Components that are commonly identified by letters are called Semi-conductor devices examples are diodes and transistors. It has not been extensively used for ICS because of the difficulty in classifying the very great variety of I.C.s.

The first letter indicates the type of Semi-conductor material used;

- A - Germanium
- B - Silicon
- C - Gallium arsenide
- D - Indium antimonide
- R - Photo Conductive Material. No Junction formed.

The second letter indicates construction or use of the device;

- A - Indicates that it is a detector diode, high speed diode mixer diodes e.g. BAT54.
- V - Variable Capacitance diode.
- E - Transistor for Audio frequency application (not power output)
- D - Power transistor for audio frequency application
- E - Means it is a tuned diode
- F - Transistor for radio frequency
- L - Power radio frequency

- P - Photo Sensitive devices or detector or radiated energy
- Q - Radiating diode
- R - Resistor or other Switching device (low power)
- S - Switching transistor (Not Power type)
- T - Thyristor or other controllers (with high power)
- U - Power transistor for Switching application.
- X - Multiplier diode such as Varactor diode or varicap.
- Y - Rectifier diode.
- Z - Voltage Reference or Regulator diode.

The Serial number which consists of one letter U, X, Y, Z with two figures, simply means, it is a device for professional used not available to amateur, example, using BFY52,

- BFY 57
- ACY 17
- BFX 84

The Serial number consists of 3 figures intended primarily for used in consumer electronic such as radio, television, tape-recorder, audio-amplifier etc.

* VARICAP
 A device that act as variable capacitor or voltage regulated diode.
 In electronic circuit, a variable diode is a voltage-biased pin junction. Its capacitance is controlled by the reverse-biased voltage applied to it. It is used in a place where a variable capacitor is required. It is controlled with the help of a variable voltage source.
 * In electronic circuit, a variable diode is a voltage-biased pin junction. Its capacitance is controlled by the reverse-biased voltage applied to it. It is used in a place where a variable capacitor is required. It is controlled with the help of a variable voltage source.

IDENTIFYING COMPONENTS USING LETTERS

EUROPEAN TYPE;

The European type numbers gives us much more information, and it consist of 2 or 3 letters followed by a number previously discussed. The first (1st) letter tell us the material used. for example A-for germanium or B-for silicon etc.

The second (2nd) letter tell us what ~~type~~ of transistor we are working with or have, ~~for~~ instance, BC would indicate a silicon ~~for~~ general purpose transistor etc.

The third (3rd) letter is often used when the transistor has been developed for industrial use, as distinct from entertainment. The number next which follow indicates the stage of development. A high number means a recent type device.

AMERICAN TYPE;

American type consist of a prefix 2N, 1N, followed by a Serial number for ~~the~~ given time. 2N signifies that the device is a transistor. 1N means it's a diode, the number been the registration number means nothing e.g. 1N4148, diode, 2N 3055 - Power transistor, and 2N4044 - transistor.

JAPANESE TYPE;

Japanese numbering always indicated with 3S followed by a letter A, B, I, E, or D and a Serial number of 3 or 4 figure e.g. 3S All 2S, AS and 3SBS series are PNP transistors.

2.3 All JSE, JSD series are NPN transistor. Note that all actual type-number printed on the transistor omitted the 28.

Also note that, a lot of transistors are now available in the market with the type number already described example; OK870, GET 12, NKT 713, MDE 205, OC 71, TP 30, 31 etc Note; 2N169 is MOS FET Transistor.

Tip 2 is a silicon power transistor PNP

Tip 30 is a Silicon Power transistor NPN.

COMPONENTS Commonly Used In Electronic Circuit

RESISTORS: Resistors in an electronic circuit are used for many purposes but in all cases their property is to restrict the flow of current in the circuit. Every electronics project used a number of resistor and they are probably used in larger quantities than any other type of component.

The value of the device is usually shown by a system of color coding, with resistors of this nature having four color bands around its bodies. The first two bands indicate the first two digits of the value and the third band is the multiplier. The fourth band indicates the tolerance of the component. If occasionally you come across a fifth color band. The first band will be salmon pink in color, this indicate that the color is highly stability type.

Another form of resistor coding is sometimes used, this consist of combination of letters and numbers which are marked on the body of the component. Examples are;

1R0J = 10 Ohms 5%	5R6K = 5.6 Ohms 10%
10RF = 10 Ohms	56RJ = 56 Ohms 50%
K10K = 100 Ohms 10%	K56J = 560 Ohms 5%
1K0J = 1K Ohms 5%	5K6G = 5.6 K Ohms 2%
10KG = 10K Ohms 2%	56KM = 56K Ohms 20%
1M0F = 1M	M56K = 560K Ohms 10%
10MK = 10 Ohms 10%	5M6M = 5.6M Ohms 20%

The last letter is always the tolerance as follows below;

$$F = \pm 1\%$$

$$G = \pm 2\%$$

$$J = \pm 5\%$$

$$K = \pm 10\%$$

$$M = \pm 20\%$$



Capacitors

This are usually described by their dielectric and May vary in Capacity: from a few pico-farads to many thousands of Micro-farads, and have voltage ratings, from a few volts to many kilovolts. Despite all these variations, the device, Capacitor in Ct diagram are designated by One symbol, unless they are polarised e.g (electrolytic).

The values of Capacitors are express in farads, and its unit is named after Faraday. Capacitor values are normally expressed in terms of Micro-farads, Nano-farads, or Pico-farads. A thousand of Micro-farad, and a Pico-farad is equal to one thousand of a nano-farad. Micro-farad is abbreviation as M while Micro-farad MFd or Nano-N. Pico is P. Also Capacitor value are often expressed in terms of NF or PF.

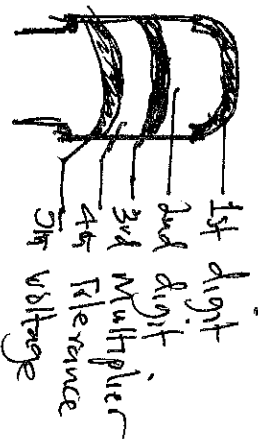


fig a) C280 TYPE CAPACITOR CODE

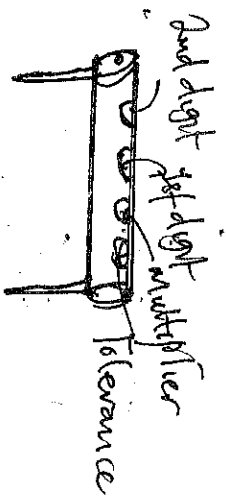


fig c. Taperule CERAMIC CAPACITOR CODE

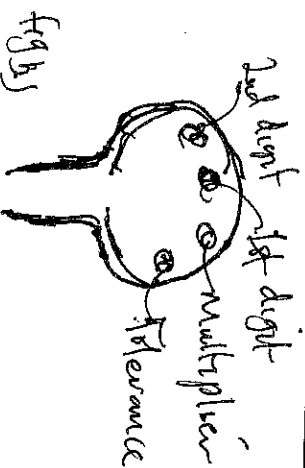


fig b) DISC CERAMIC CAPACITOR CODE

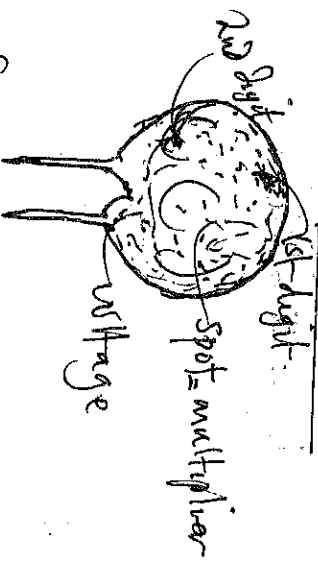


fig d. Tantalum BEAD CAPACITOR CODE


The element shown in a Schematic are refer to by letters and for numbers. The letters are usually abbreviated from a complete name e.g resistor are marked by letter R, and Capacitors are C etc.

Ordinarily paths for signal or energy are shown from start to end. If however lines may be broken off (as it is usually done for filament circuits) At the break, the line is terminated in an arrow head and bears an inscription stating its destination. So that a Schematic will not look too crowded. Groups of lines may be shown by a single line if an electronic system has several sub-system or devices, it is usually easy to draw-up a separate schematic for each of them.

GUIDE LINE FOR DRAWING A WELL ARRANGED SCHEMATIC DIAGRAM;

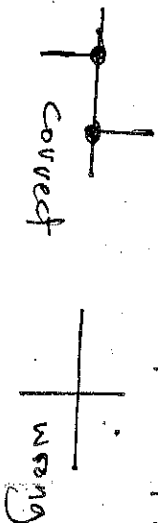- 1) When Conductors ~~meet~~^{are} crossing in a schematic diagram, they appropriately do so at the right angle 
- 2) Where one conductor joins another, the joint must be indicated by a dot drawn with a diameter of about 1mm. If the joint is a T-joint, at one point only.  meaning that only one dot ~~is~~^{must} be used.
- 3) If the joint is double-T (or cross joint), the end of the lines (representing the joining conductors) are displaced side ways at one angle 45° at a distance of about 3mm.

and a dot is placed at point of each joint.



4.) Connection to Circuit Components are always made a small distance from the components symbols and not right at the Component Symbol.

5.) The Main rule in the layout of a Schematic diagram is that Signal flow must be from left to right or from top to bottom (or a combination of both if possible).


6.) Understand the functional Assembly and identify each Component that makes up the Circuitry.

7.) Ensure that all Components on the Circuit are included in the Schematic diagram and well fixed in their proper location, and they are all lettered & numbered.

8.) Avoid usage of different Symbols for the same device.

9.) Transistor and tube symbols should be aligned horizontally.

5

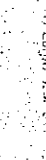

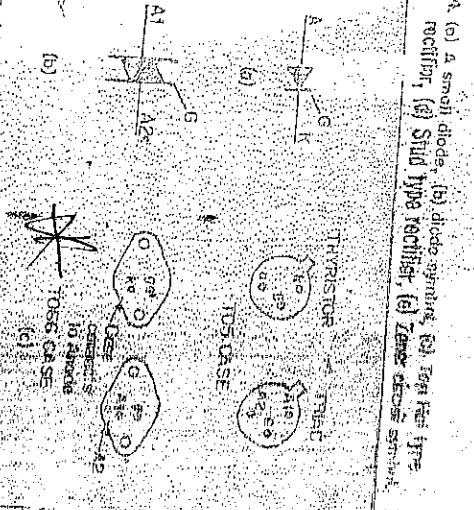
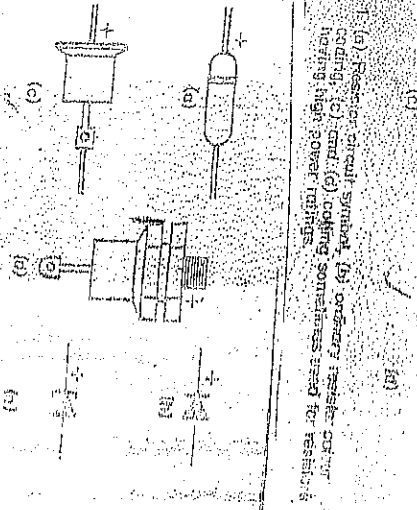
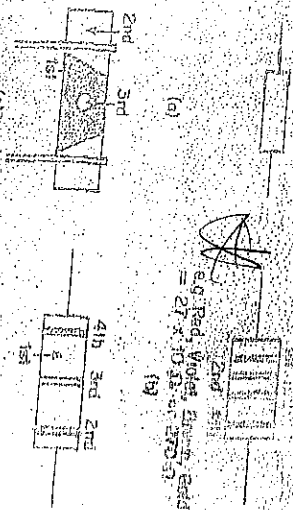


Fig. 7. (a) Thyristor circuit symbol, (b) Thyristor circuit symbol, (c) connection diagram.

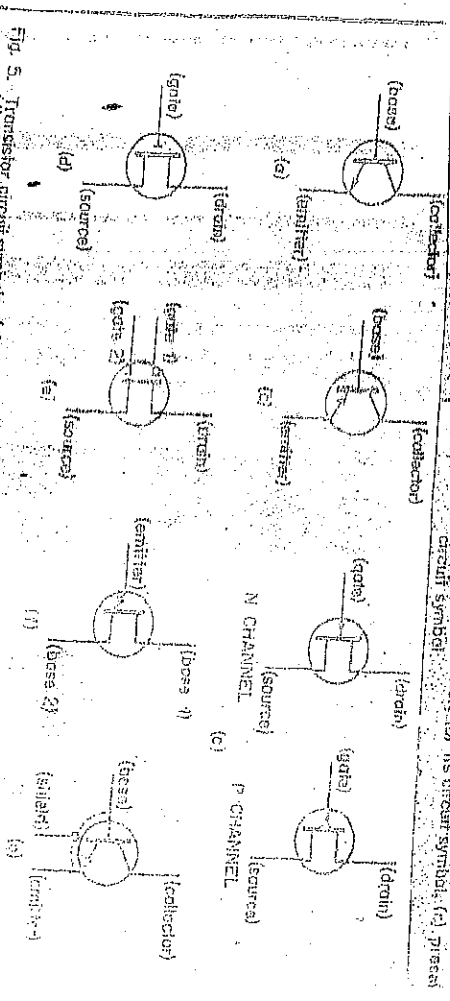


Fig. 5. Transistor circuit symbols: (a) NPN bipolar, (b) PNP bipolar, (c) NPN MOSFET, (d) PNP MOSFET, (e) NPN MOSFET, (f) PNP MOSFET.

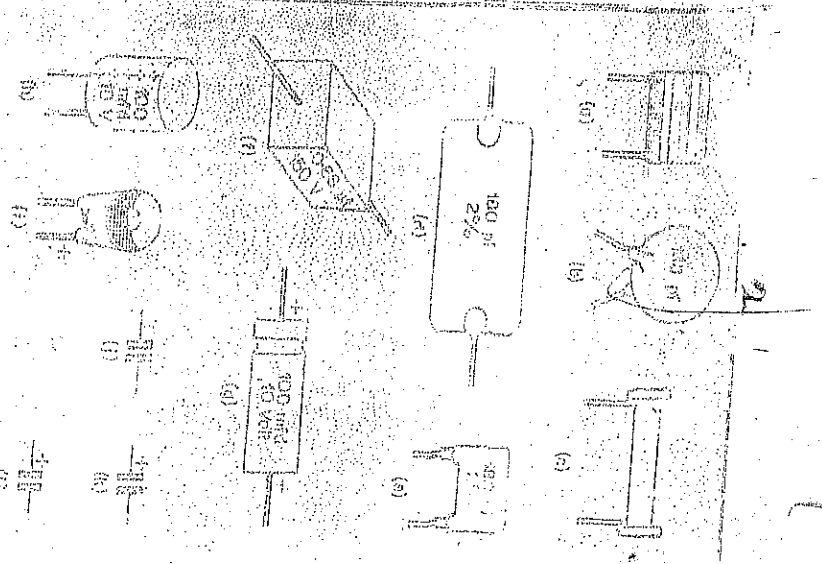


Fig. 6. (a) A potentiometer, (b) its circuit symbol, (c) potentiometer circuit symbol.

FORMS DEFINITION & APPLICATION OF DIAGRAMS

BLOCK DIAGRAM:

32

DEFINITION: This is simply defined as a diagram of a system, instrument which selected portion are represented by a given annotated boxes and interconnected ~~with~~ lines or wires.

A block diagram is a graphical representation of a system, which provides a functional view of the system, ~~and~~ gives a better understanding of a system's functions and also help create interconnections within it. Block diagrams derive their name from the rectangular elements found in this type of diagram. They are used to describe hardware and software systems as well as to represent processes.

Block diagram are described and defined according to their function and structure as well as their relationship with other blocks. The function performed by each unit is stated in verbal form inside the block. The relationship to one another is indicated by appropriately connected lines and arrows, the arrow-heads point from the controlling ^{responsible} towards the controlled unit.

WHY ARE BLOCK DIAGRAMS IMPORTANT?

A block diagram is an essential method used to developed and describe hardware or software systems as well as represent their workflows and processes.

- They are used in electronics to represent systems in the trucking industry.

- Block diagrams are generally used when the visualization of information or control flows is important, or when processes are involved.

In this way, we can represent complex algorithms or flows components within a large system, as well as of information or communication among individuals components within a large system as well as it. For example in a facility designed for mass production.


STEPS TO TAKE IN DRAFTING BLOCK DIAGRAM: 33

- 1- Understand the functional Assembly of the circuitry.
- 2- Identify the various stages involved.
- 3- Study the signal flow left to right or from top to bottom.
- 4- The input and output must be shown or must be determined.
- 5- All the sub-connections from feedback loops must be clearly identified and indicated.
- 6- The engineer designer usually begins the design of an electronic devices by laying out a block-diagram. This block diagram is then used as a guide while the designs circuit represented by various blocks in the system.

APPLICATION: In design work, block diagrams are drawn up prior to all other forms. In service, they give an over all idea about the operation of the equipment.

To illustrate this, Consider the block diagram of an audio amplifier, assume the input signal will be from Microphone or Phonogram, Pick-up, the o/p signal must be large enough to actuated a loudspeaker. A typical diagram of this device can be sketched as shown below;

BLOCK DIAGRAM OF AN AUDIO AMPLIFIER

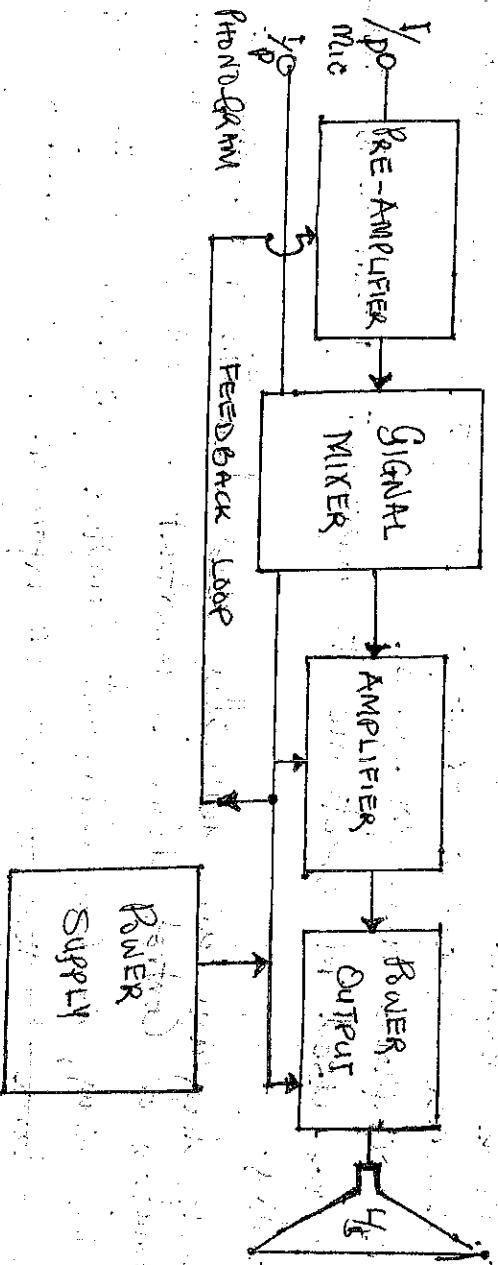

SCHEMATIC DIAGRAM (ELEMENTARY), 34

A Schematic diagram is a visual representation of the elements of a system (ccts) using abstract, graphic symbols rather than realistic pictures. It is defined as a picture that represents the components of a process, device or other object using abstract, often standardized symbols and lines.

A Schematic diagram is basically a fundamental two dimensional circuit representation showing the functionality and connectivity in different electrical components. It is vital for a PCB designer to get familiarized with the schematic symbols that represent the components on a schematic diagram. Although schematic diagrams are commonly associated with electrical ccts, many examples can be found in other industries. Schematic diagram only "depict" the significant components of a system, though some details in the diagrams may also be exaggerated or introduced to facilitate the understanding of the system.

They do not include details that are not necessary for comprehending the information that the diagram was intended to convey. For example, in a schematic diagram depicting an electrical cct, you can see how the wires and components are connected together, but not photographs of the circuit itself.

More simply a Schematic diagram is a simplified drawing that uses symbols and lines to convey important information and they are most commonly associated with electronic components in electrical circuit and they are also called wiring diagram or cct diagrams.

STANDARDS FOR SCHEMATIC SYMBOLS

IEC 60617: International Electrotechnical Commission has issued this standard. It is based on the older standard. British standard BS 3939. This database includes over 1750 schematic symbols.

ANSI STANDARD Y32: American National Institute (ANSI)

This provides a variety of specialized symbols, originally used for aircraft applications. A series of minor changes performed on this standard has made the existing document aligned with IEC.

APPLICATION:

A schematic (elementary) diagram serves as a basic for other diagrams and drawings. It gives an insight in operation of individual circuit and components. Useful in testing, repair and alignment and services.

* SIGNAL FLOW (FUNCTIONAL DIAGRAM)

In functional diagram, a diagram tracing the passage of signal in an equipment diagram or part thereof.

APPLICATION! A signal flow diagram gives an insight to operation principle of a system. It is also useful in the testing, alignment and repair of the equipment or instrument.

* WIRING (INTERNAL CONNECTION DIAGRAM)

This is simply a diagram that shows the internal connection of a system and / with details and accessory items such as cable drive, type terminals blocks, connection leads etc.

APPLICATION! This form of diagram is used when putting a system or equipment into service.

* SYSTEM DIAGRAM

This is basically a diagram that relates the sub-system of a system according to functions they perform in service.

APPLICATION! A system diagram is used to get a general idea about the sub-systems and a system as a whole during installation, inspection or operation.


* LAYOUT DIAGRAM

This is a diagram that shows all the components of an equipment in their physical relation to one another.


APPLICATION! A layout diagram is used in working out engineering drawings and also when installing or maintaining an equipment.

... It also helps in the process of design.

SCHEMATIC DIAGRAM OF A SIGNAL TRACER

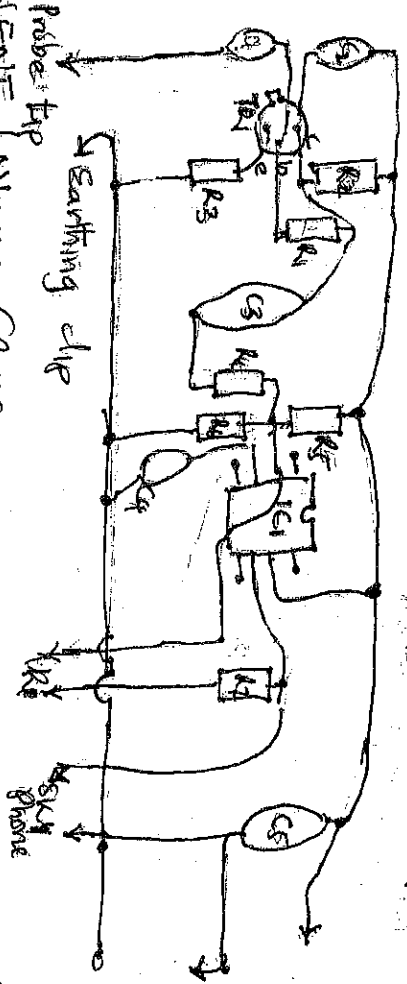

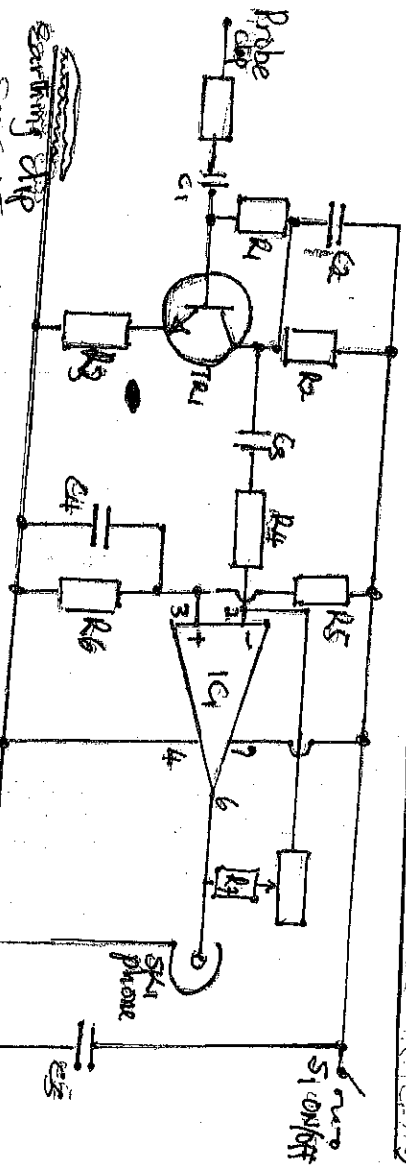COMPONENTS LAYOUT (ROUGH SKETCH OF A SIGNAL TRACER)



SCHEMATIC DIAGRAM OF A SIGNAL TRACER

COMPONENTS LIST OF THE ABOVE DIAGRAM

R1	3M3
R2	10K
R3	1K
R4	20K
R5	39K
R6	39K
R7	20K
C1	22nF
C2	10nF
C3	20nF
C4	100nF
C5	100nF
U1	2m2-11N
IC1	LF 351
TA1	6C 109C
SP1	Single Pico (SPST)

* EXTERNAL CONNECTION DIAGRAM

37

This diagram simply shows the external connections of a system or equipment and contain details and accessories. Similar to those in an internal connecting diagram.

APPLICATION: This form of diagram is used when putting a system or equipment into service.

* LOGIC DIAGRAM

Logic diagram is a diagram representing all the logical elements and their interconnection without necessarily expressing constructing or engineering details.

In Logic diagrams, every symbol represent a unique logical device. It gives more idea about the circuit more than a block diagram. Each straight line in a logic represent a conductor.

In design work, block diagram is drawn prior to all other forms in service, they basically give an overall idea about the operation of the equipment.

PROCEDURE / STEPS IN DRAFTING LOGIC DIAGRAM

- Project or have a sketch of the schematic with all the symbols
- You should be able to recall what each symbols means
- You should be able to know dimension for each symbols
- Note that signal flow from left to right.
- Start by drawing input ward matrixes.
- Should tie the devices to the input terminals.
- Identify the number of input and output required.

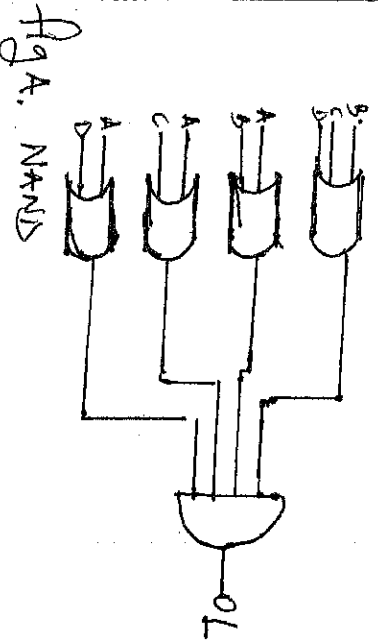


Fig A. NAND

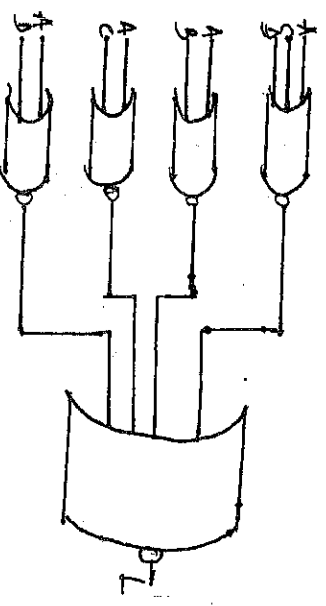


Fig B. NOR

Logic Diagrams:

What's ELECTRICAL CIRCUIT-BOARD?

A circuit board is a physical piece of technology that allows for the assembly of electrical or data circuits on a horizontal layer of material. It is the heart of the electronic circuitry that controls the circuitry of the device and provides power to the device.

The circuit board is a physical piece of technology that allows for the assembly of electrical or data circuits on a horizontal layer of material. It is the heart of the electronic circuitry that controls the circuitry of the device and provides power to the device.

What's a PCB (Printed Circuit Board)?

A PCB is a physical piece of technology that allows for the assembly of electrical or data circuits on a horizontal layer of material. It is the heart of the electronic circuitry that controls the circuitry of the device and provides power to the device.

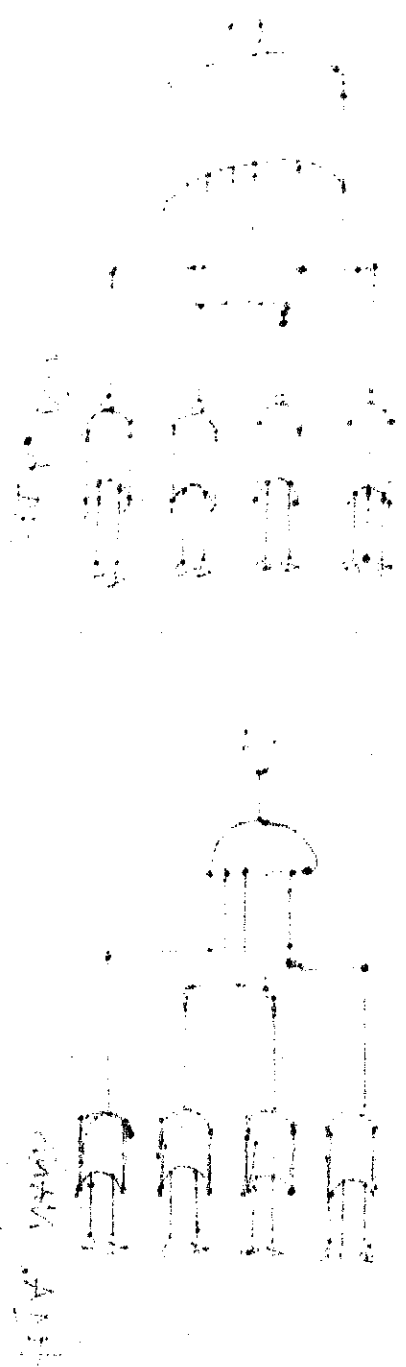


Diagram of a PCB

Circuit Construction

38

Types of Circuit Board

* SOLDERLESS BREADBOARD: This type of circuit board is used temporary, which therefore required "no soldering" in its process or in use.

This is a way of making a temporary circuit, for testing purposes or to try out an idea. No soldering is required and all the components can be re-used afterwards. It is easy to change connections and replace components. Almost all the electronics club projects started life on a breadboard to check that the circuit worked as intended.

USES OF BREADBOARD


Solderless breadboard is basically used in the laboratories for low powered project as preparation board so as to confirm that the project is effectively working before transferring it or using the permanent board. As it is called, this board needs not to be soldered because clips are attached below each hole as directed by the manufacturer. Base on the fact that it is used to make-up temporary circuits for testing or to try out an idea, parts will not be damaged so they will be available to re-used afterwards.

CONNECTIONS ON BREADBOARD

Breadboards have many tiny sockets (called "holes") arranged on 0.1" grid. The leads of most components can be pushed straight into the holes. ICs are inserted across the central gap with their notch or dot to the left.

- Wire links Can be made single-core Plastic-coated wire of 0.6mm diameter (the standard size). Stranded wire is not suitable because it will crumple when pushed into a hole and it may damage the board if strands break off.

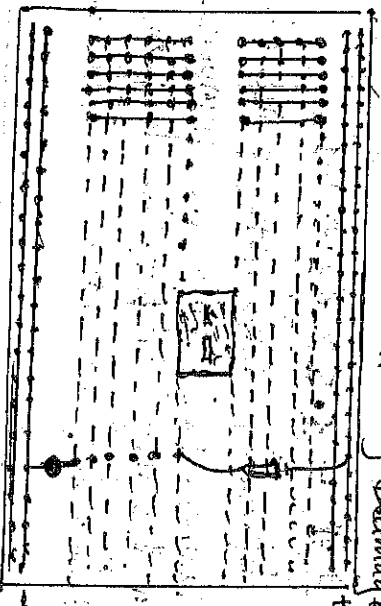The diagram shows how the breadboard holes are connected



The top and bottom rows are linked horizontally all the way across as shown by the red and black lines on the diagram. The power supply is connected to these rows, + at the top and 0V (Zero volts) at the bottom.

I suggest, using the upper row of the bottom pair for 0V, then you can use the lower row for the negative supply with circuits requiring a dual supply (example +9V, 0V, -9V). The other holes are linked "vertically" in blocks of 5 with no link across the centre as shown above, by the blue lines on the diagram. Notice how there are separate blocks of connections to each pin of ICs.

LARGE BREADBOARDS

On larger breadboard, there may be a break halfway along the top and bottom power supply rows. It is a good idea to link to link across the gap before you start building the circuit, otherwise, you may forget and part of your circuit will have no power.

BUILDING A CIRCUIT ON BREADBOARD


Converting a circuit diagram to a breadboard layout is not straightforward because the arrangement of components on breadboard will look quite different from the circuit diagram.

When putting parts on breadboard you must concentrate on their connections, not their positions on the circuit diagram. The IC (chip) is a good starting point, so place it in the centre of the breadboard and work round it pin by pin, putting in all the connections and components for each pin in turn.

The best way to explain this is by these examples, so the process of building this 555 timer circuit on breadboard is listed step by step below.

The circuit is a monostable which means, it will turn on the LED for about 5 seconds when the 'trigger' button is pressed. The time period is determined by R_1 and C_1 and you may wish to try changing their values. R_1 should be in the range 1k Ω to 1M Ω .
Time Period (s) = $1.1 \times R_1 \times C_1$.

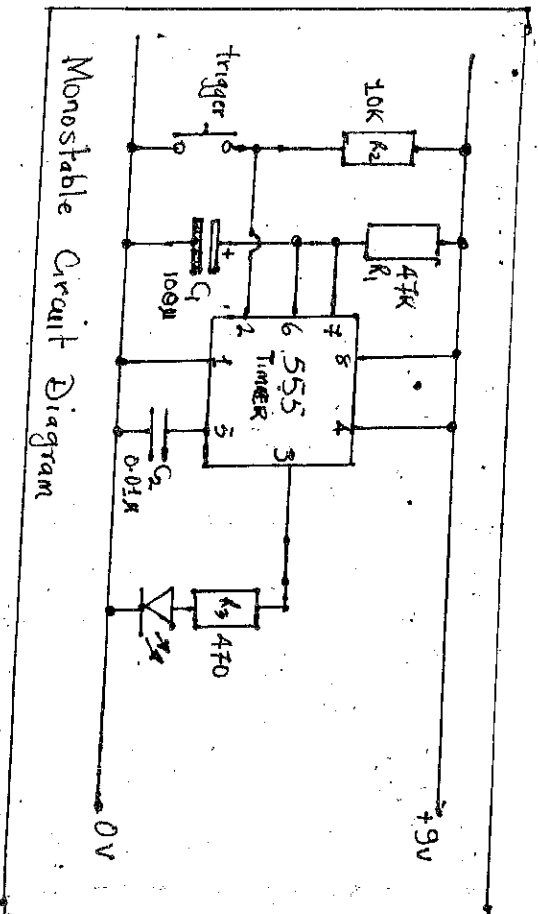For further information, take note of the 555 Monostable IC Pin Numbers! IC Pins are numbered anti-clockwise around the IC starting near the notch or dot. The diagram shows the numbering for 8pin and 14pin ICs, but the principle is the same for all sizes.



Monostable Circuit Diagram


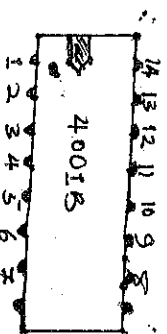


fig 14 pin IC

COMPONENTS WITHOUT SUITABLE LEADS

Some components such as switches and variable resistors do not have suitable leads of their own, so you must solder some on yourself.

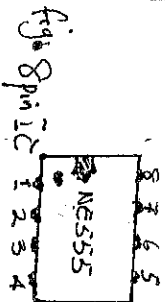Use single-core plastic coated wire of 0.6mm diameter (the standard size). Stranded wire is not suitable because it will crumple when pushed into a hole and it may damage the board if strands break off.



IMPORTANT KEYNOTE;

- Check all the connections carefully
- Check that parts are ~~the~~ correctly wired round (LED and 100µF capacitor)
- Check that no leads are touching (unless they connect to the same block)
- Connect the breadboard to a 9V supply and press the push switch to test the circuit.
- If your circuit does not work as required disconnect (or switch off) the power supply and very carefully re-check every connection against the circuit diagram.

Solderless breadboard usually cannot accommodate Surface-Mount Technology (SMD) or non 0.1" (2.54mm) gnd. spaced components, like for example those with 2mm spacing. Further, they can not accommodate components with multiple rows of connectors. If these connectors don't match the DIL layout (it's impossible to provide correct electrical connectivity). Sometimes small PCB adapters (breakout adapters) can be used to fit the component on such adapters. Carry one or more of the non-fitting components and 0.1" (2.54mm) connectors in DIL layout. ~~larger~~ ~~the~~ components are usually plugged into a socket, where the socket was soldered onto such an adapter. The smaller components (e.g. SMD resistors) are usually directly soldered onto such an adapter. The adapter is then plugged into the breadboard via the 0.1" connectors. However, the need to solder the component or socket onto the adapter contradicts the idea of using a solderless breadboard for prototyping in the first place. Therefore, complex circuits can become unmanageable on a breadboard due to the large amount of wiring necessary.

PLAIN MATRIX BOARD OR PLAIN VERO BOARD

Plain matrix board is often referred to as plain Vero board which is the trade name of Veroboard LTD.

However, it is produced by other manufacturers; matrix board which consists of a sheet of insulated material (veroboard paper) which has been divided with a matrix of small holes. These boards are available in various sizes and in two pitches i.e. (2.54mm = 1mm and 3.8mm (0.15m)) the 3.8mm (0.15m) matrix type is for general purpose or used. The reason for this is that the most popular ICs have pins that are spaced on a 2.5mm.

To suit a particular circuit and component layout, so that they do not have a matrix of holes, these are only drilled where components are actually going to be mounted.

PLAIN MATRIX BOARD LAYOUT

42

- * Almost invariable the components are mounted on the matrix panel using the same layout as they used in the circuit diagram.
- * You can therefore keep the practical layout as much like the est layout as possible, or can make a few simple modifications which will provide a more compact layout without any crowding of components.
- But avoid the necessity to insulate any of them with PDC sleeving. ~~This~~ This is usually the case if the physical layout been kept as much the same as the theoretical one, but not likely to be the case of the physical layout, been nothing compare like the circuit.
- * The normal way of mounting a circuit board is to bolt it to the case of the equipment and for small panels it is usually sufficient to use two mounting points.
- * Note that, three rows of used holes should be left out to provide space for these holes.

PLAIN MATRIX BOARD CONSTRUCTION

- By construction, firstly cut out a panel of the correct size. It is easier to cut along a row of holes rather than between rows.
- A junior hack-saw or a full size type can be used for that process.
 - Any mounting holes can be drilled and in case they can be made using a 3.2mm drill-bit, so that they will accept m3 mounting bolts.
 - Next, the components ^{that} are mounted on the panel, their lead out are bent over at right angle on the underside of the board, they ~~are~~ ^{should} be wired together in their correct method.
 - Connect first the component to the negative supply rail (or positive supply rail in case of positive earth equipment) before wiring up the rail, one by one. The other components are mounted and soldered into circuit.
 - Another method is to start off mounting all the components and then cut their lead out, wires to length and solder them together as necessary.

Point-to-Point Soldering


443

The process of soldering is simply the end of lead-out wires (or tags), etc, with solder which is also simply known as Tinning. When point-to-point wiring is used (lead and tags are soldered directly to one another. It is advisable to tin all tags and leads before attempting to complete any joints. Though this tinning is less important on printed circuit board unless a lead or tag is badly contaminated whatever method is used, always make sure that plenty of solder is used on each joint when carrying out point-to-point wiring.

PRINTED CIRCUIT BOARD

Printed circuit boards basically consist of thin sheet of an insulation material such as S.R.P.P or Fiber-glass, and on one side of the board, the presence of copper exists. PCBs have copper tracks connecting the holes where the components are placed. They are designed specially for each circuit and make construction very easy. However, producing the PCB requires special equipment so this method is not recommended if you are a beginner unless the PCB is provided for you. The components are mounted on the non-coppered side of the board with their lead passing through the holes. The leads are cut to length on the side of the board, so that 1mm of lead-out is left protruding through the panel, the leads are then soldered to the copper backing.

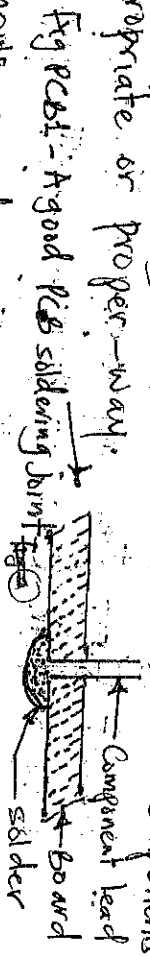The purpose of the copper backing is of course to connect components together in their appropriate or proper way.



The above diagram shows a side view of a good PCB soldered joint. Have the solder flowed tightly around the lead and over a fairly large area of copper backing. A part from providing a good electronic connection, it also provides a firm physical mounting for the component, which is very important.